




# Monolithic High Frequency GaN Switched-Mode Power Converters

Dragan Maksimovic  
maksimov@colorado.edu

Colorado Power Electronics Center (CoPEC)  
ECEE Department, University of Colorado - Boulder

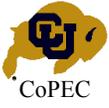IEEE PELS Chapter meeting, UC Berkeley, February 1, 2016



# Outline

---

- CoPEC: Colorado Power Electronics Center
- Introduction to wide bandgap semiconductors
- Monolithic VHF GaN converters
  - Application of interest: drain supply modulation for RFPA's
  - Half-bridge power stage with integrated gate drivers in GaN process
  - Experimental results: 10-400 MHz switching, up to 50V, >10W power
- Conclusions


# Colorado Power Electronics Center (CoPEC)

## CoPEC faculty:


Prof. Bob Erickson  
 Prof. Dragan Maksimovic  
 Prof. Khurram Afridi  
 Prof. Hanh-Phuc Le (PMIC's)  
 Prof. Zoya Popovic (RF/Microwaves Lab)  
 Dr. David Jones (Post-Doc Research Associate)

**Research and education programs**  
 in smart power electronics for energy efficiency and  
 renewable energy applications and systems

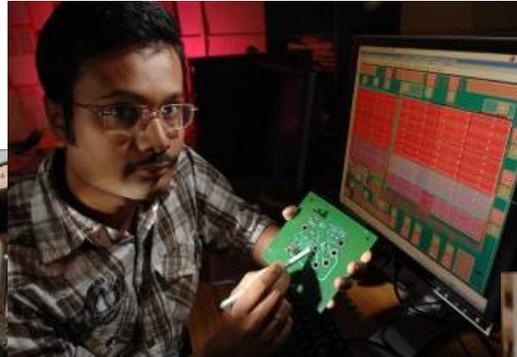*From digital power control  
 for components and systems...*



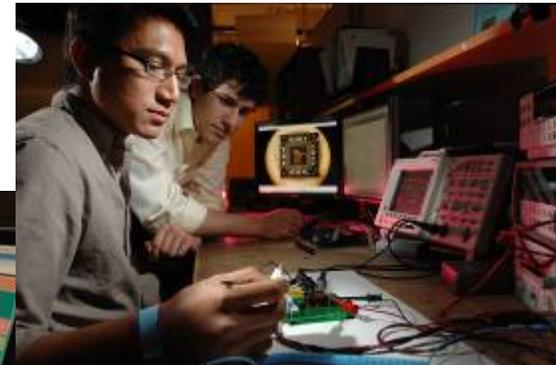*...to custom power  
 management ICs ...*



*... to energy harvesting and  
 wireless power transfer ...*



*...energy efficient lighting systems,  
 renewable energy systems, and  
 automotive (EV) applications*

## Research projects:

- Sponsored by industry via CoPEC membership
- Sponsored by industry and agencies as separately directed contract projects

# CoPEC Educational Program

## Comprehensive power electronics curriculum

- Introduction to power electronics
- Resonant and soft-switching techniques
- Modeling and control of power electronics
- Power electronics and photovoltaic systems lab
- Power electronics for electric drive vehicles
- Adjustable speed ac drives
- Analog and mixed-signal integrated circuit design



## Graduate certificates in (1) PE and (2) EV Technologies


## Courses can be taken online through

[beboulderanywhere.colorado.edu](http://beboulderanywhere.colorado.edu)

## Specialization in power electronics available through Coursera

[www.coursera.org/specializations/power-electronics](http://www.coursera.org/specializations/power-electronics)

# CoPEC Research Directions

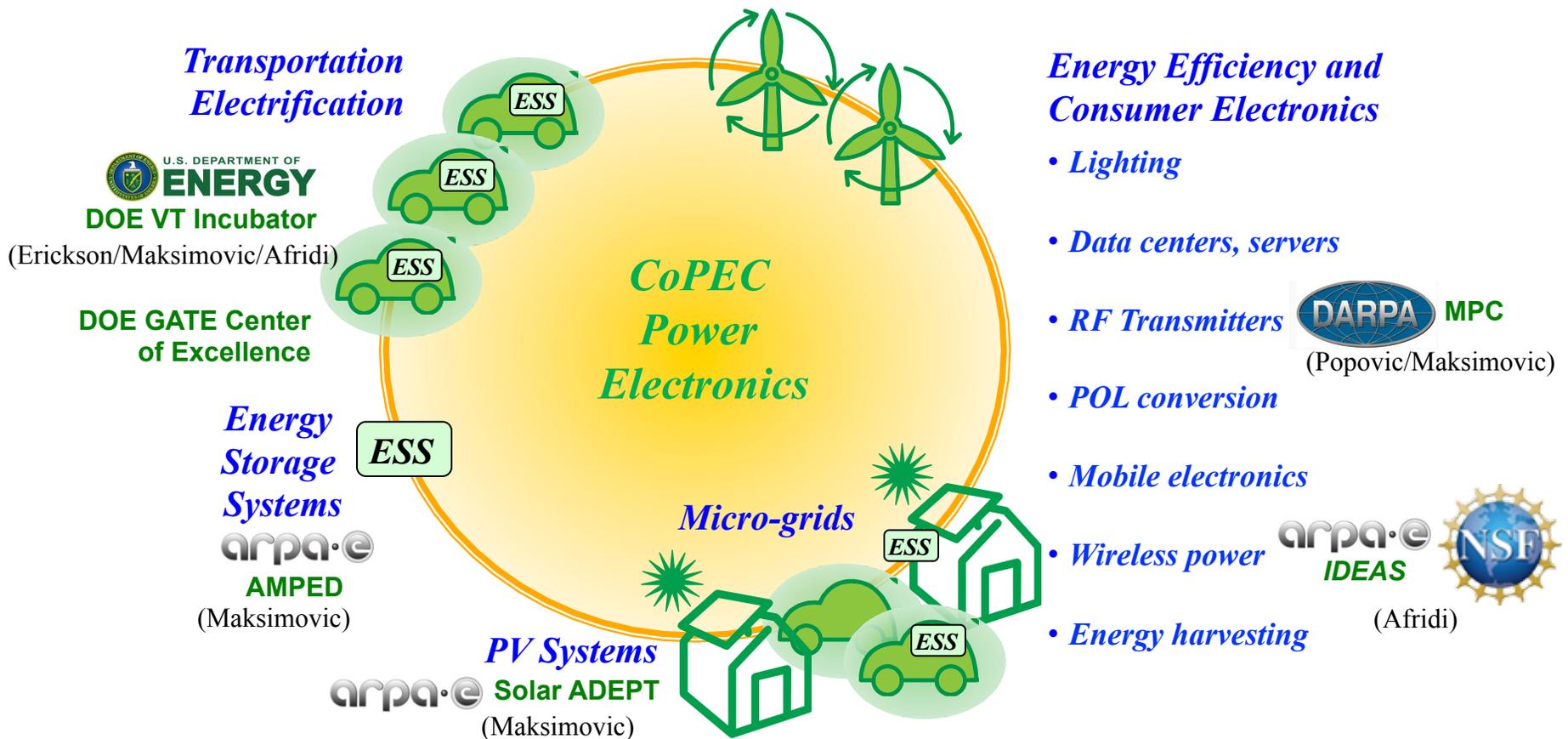

- Research projects sponsored by industry through CoPEC, and by various agencies
- Collaborations with National Renewable Energy Laboratory

# Introduction to wide bandgap semiconductors

Switch on-resistance  $R_{on}$  as a function of breakdown voltage  $V_B$

$$R_{on} = k \frac{V_B^2}{A} \frac{1}{\mu_n \epsilon_s E_c^3}$$

$A$  = device area

$V_B$  = device breakdown voltage

$E_c$  = critical electric field for avalanche breakdown

$\mu_n$  = electron mobility

$\epsilon_s$  = semiconductor permittivity

$$\frac{AR_{on}}{V_B^2} = \frac{R_{on,sp}}{V_B^2} = \frac{k}{\mu_n \epsilon_s E_c^3} = \text{Semiconductor material figure of merit (FOM) for majority-carrier devices (e.g. MOSFETs)}$$

# Comparison of semiconductor materials


Material	Bandgap [eV]	Electron mobility $\mu_n$ [cm <sup>2</sup> /Vs]	Critical field $E_c$ [V/cm]	Thermal conductivity [W/m <sup>o</sup> K]
Si	1.12	1400	$3 \times 10^5$	130
SiC	2.36-3.25	300-900	<b><math>1.3-3.2 \times 10^6</math></b>	700
GaN	3.44	900 1500-2000 (AlGaN/GaN)	<b><math>3.0-3.5 \times 10^6</math></b>	110

## Advantages of wide bandgap (SiC, GaN) power semiconductors


- Much better FOM, reduced resistive voltage drops at higher breakdown voltages
- Much reduced stored charge (MOSFET), much reduced reverse-recovery related switching losses (high-voltage Schottky diodes)
- Capability of operation at increased junction temperature




# Power electronics applications

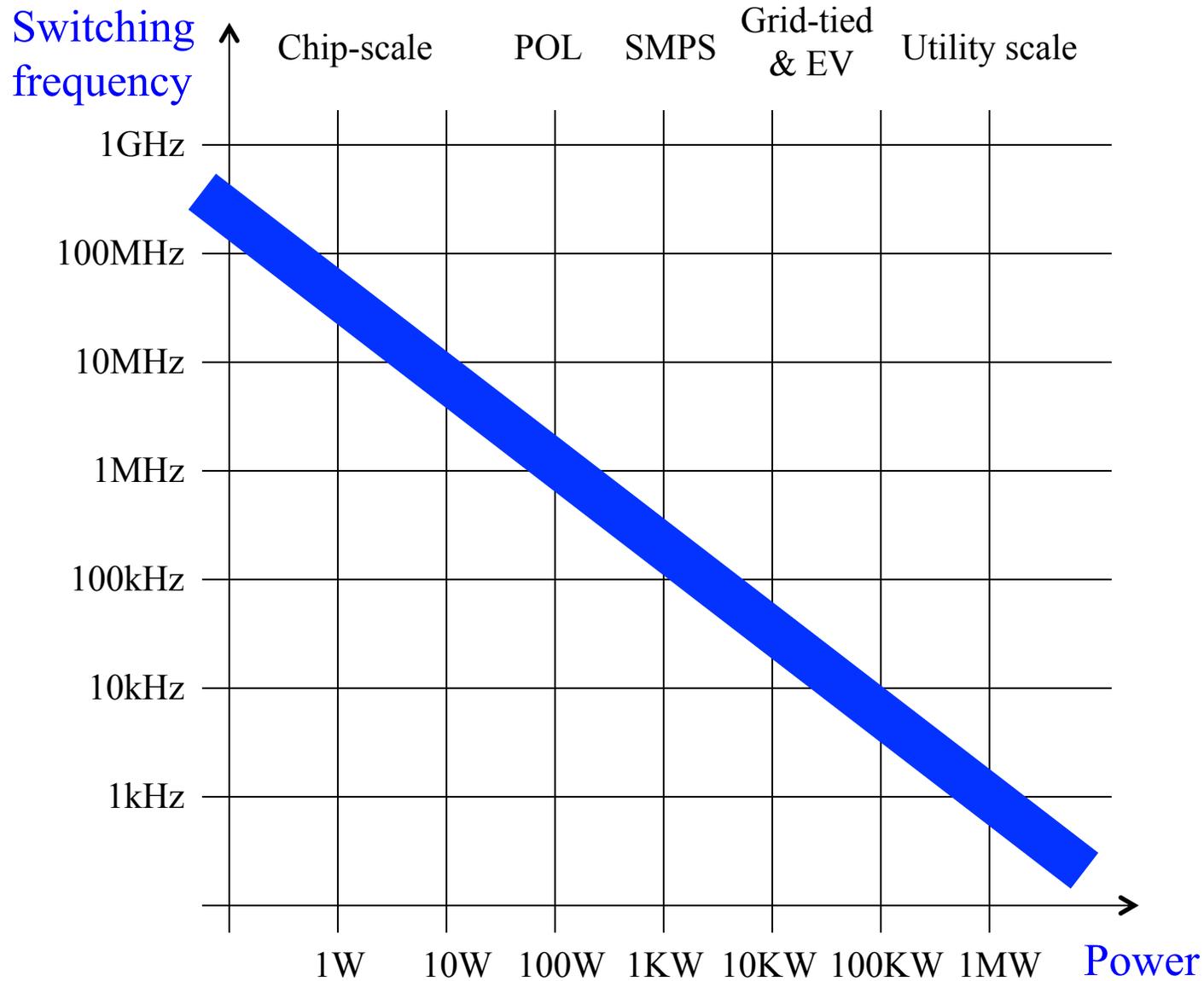
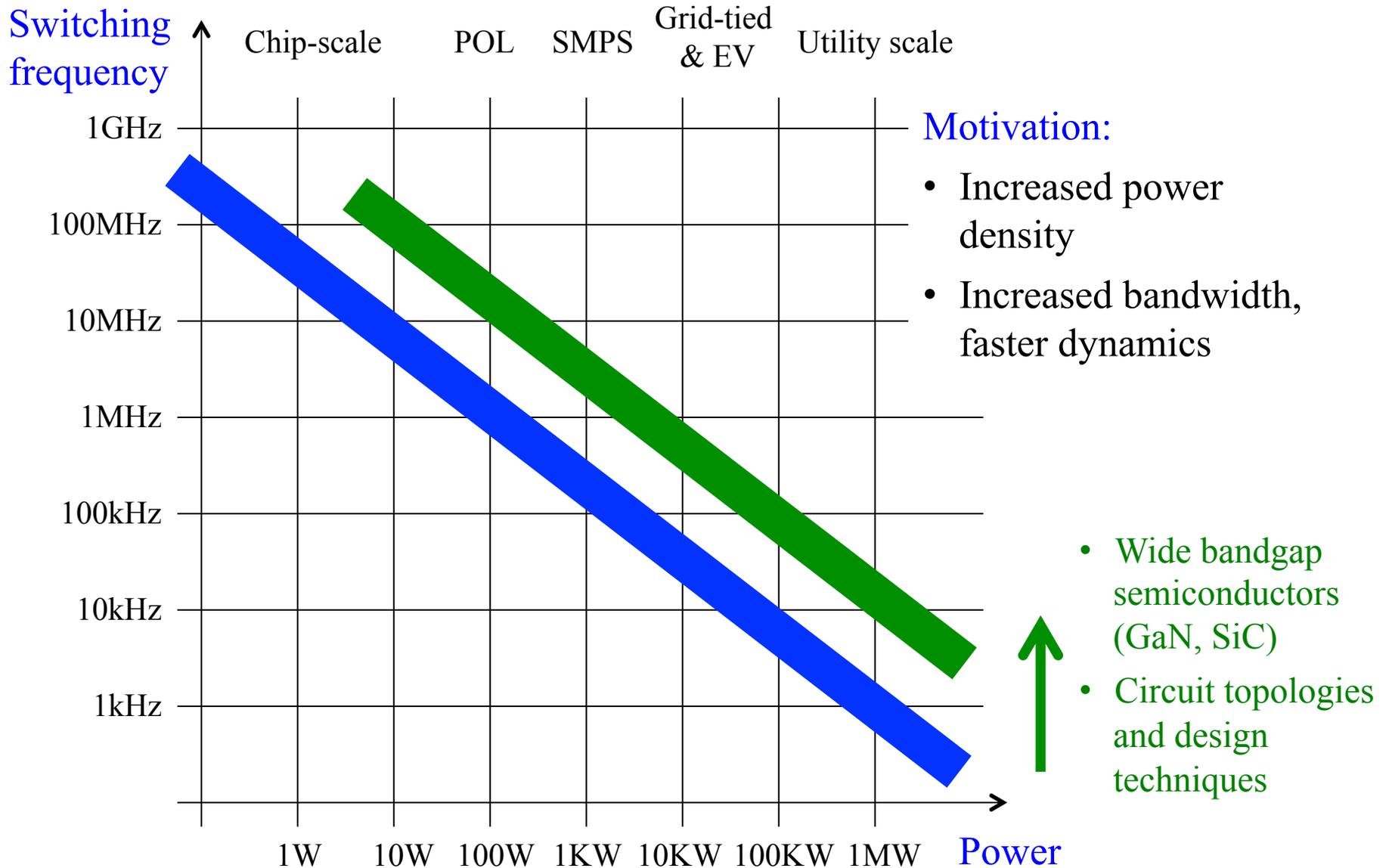
# Increased switching frequency: motivation



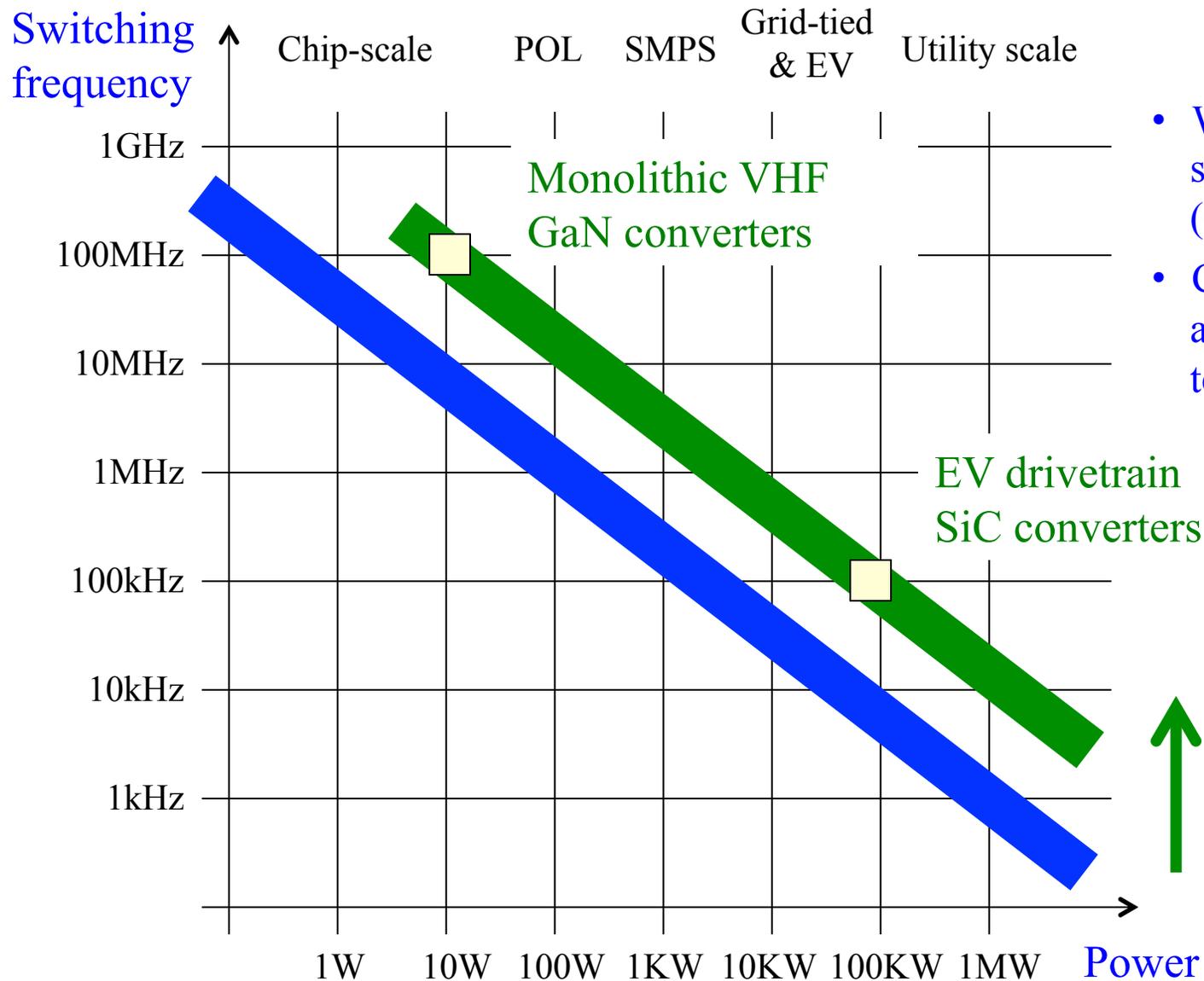
# Application examples from our recent projects



- Wide bandgap semiconductors (GaN, SiC)
- Circuit topologies and design techniques



# Application: RF transmitters

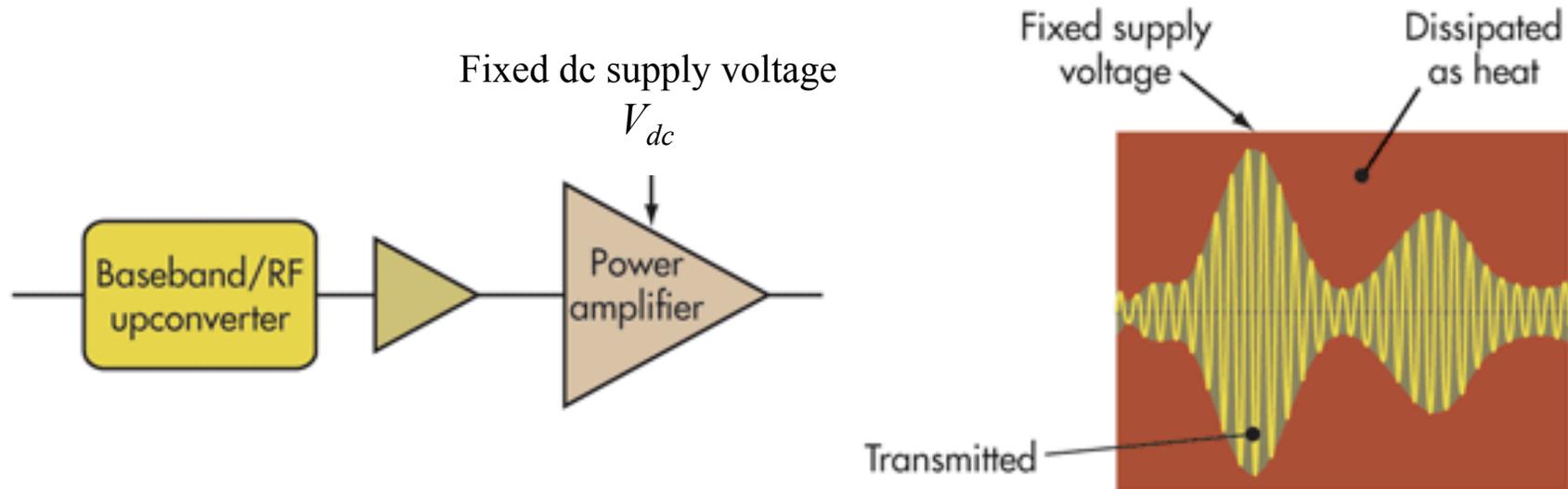

Problem: low efficiency of conventional RF transmitters in mobile, base station, and other wireless infrastructure systems

- High peak-to-average ratio (PAR) signals
- Continuous-wave (CW) or low-PAR signals at average power levels below peak

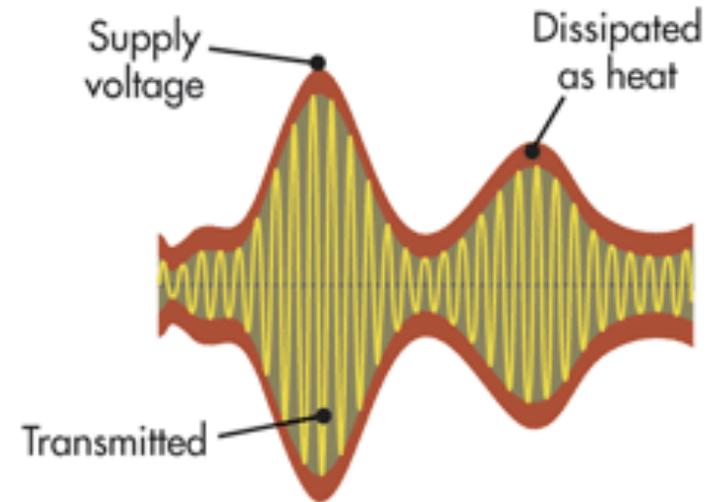
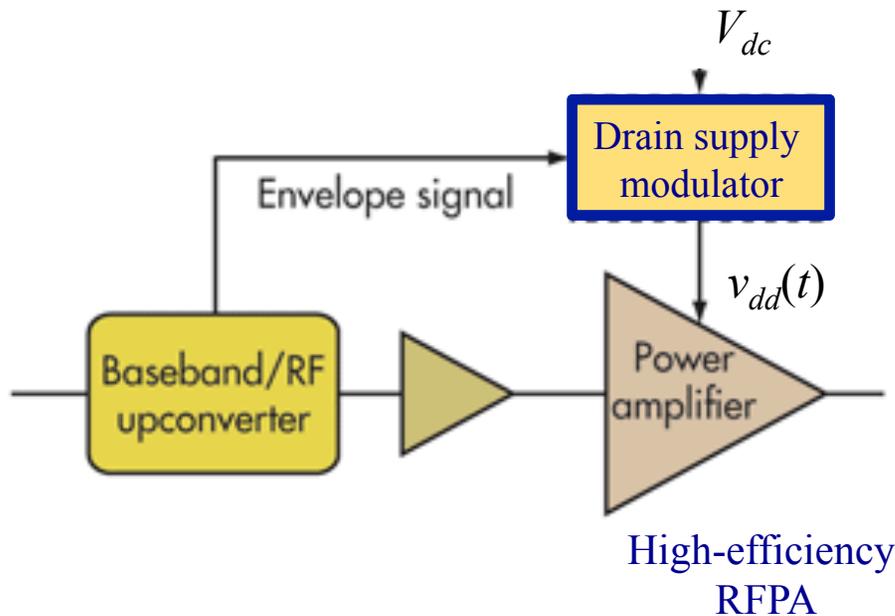
# Objective: high-efficiency, flexible RF transmitters



One possible system efficiency improvement approach:  
 “envelope tracking” transmitters based on drain supply modulation

- High-efficiency RFPA
- High-efficiency, wide-bandwidth envelope-tracking drain supply modulator
- System co-design and integration
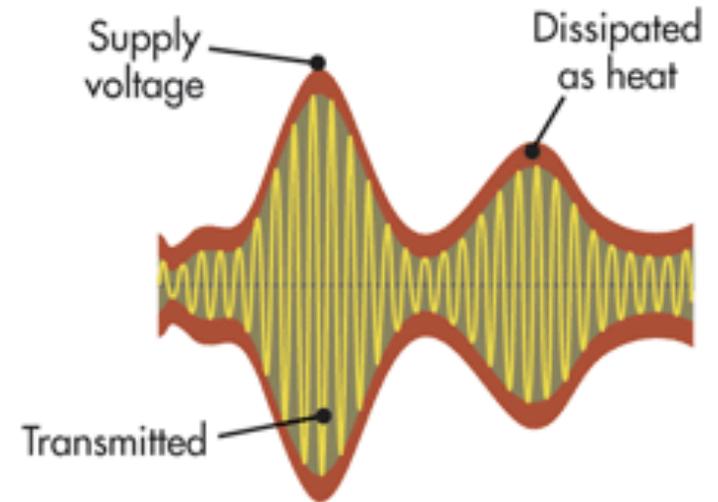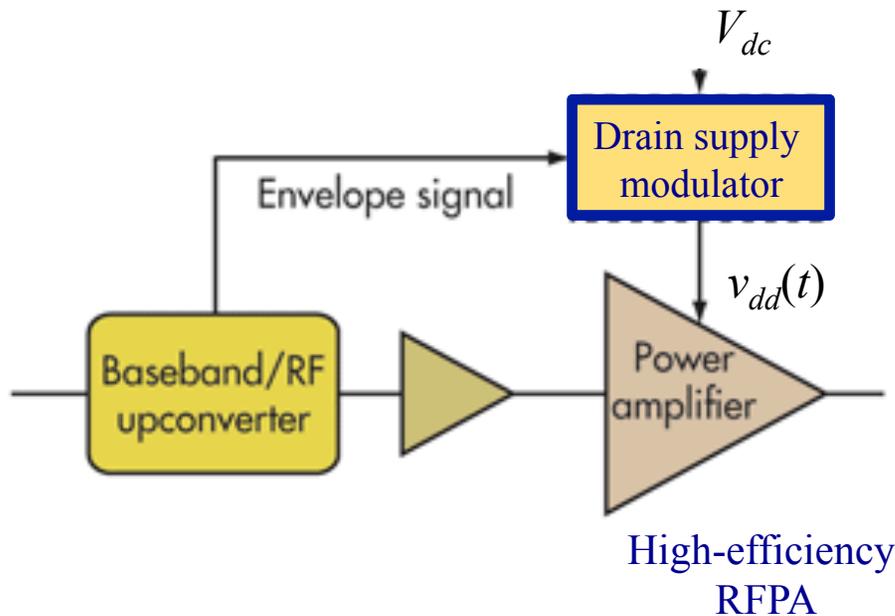
# Objective: high-efficiency, flexible RF transmitters




One possible system efficiency improvement approach:  
 “envelope tracking” transmitters based on drain supply modulation


- High-efficiency RFPA
- High-efficiency, wide-bandwidth envelope-tracking drain supply modulator
- System co-design and integration
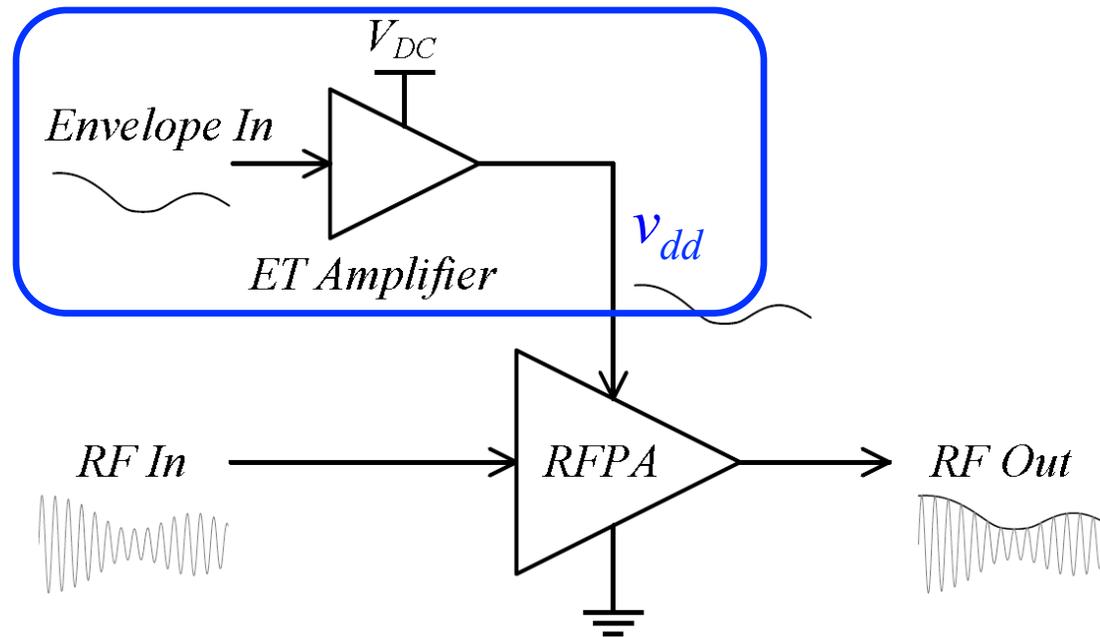
# Drain supply modulator design challenges

- Wide tracking bandwidth [ $BW_{tracking} = 10\text{'s to } 100\text{'s of MHz}$ ]
- High output voltage slew rate [ $dv_{dd}/dt = \text{several V/ns}$ ]
- High efficiency to realize system-level efficiency improvements


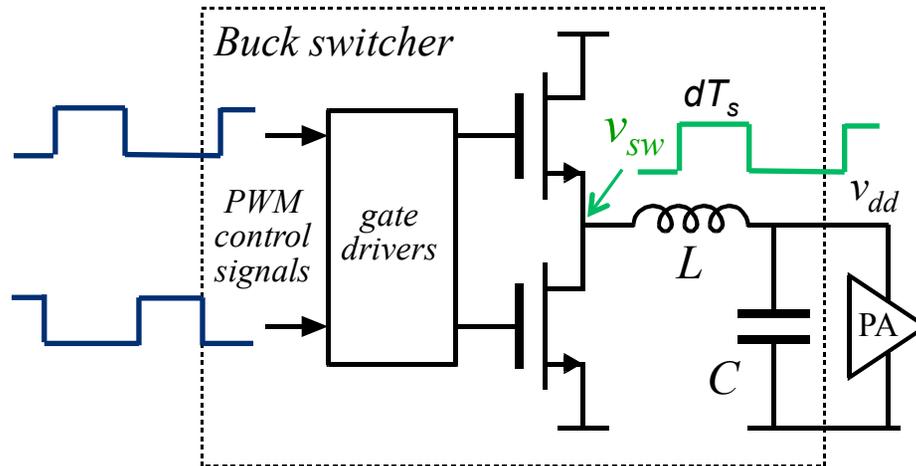
# Basic approach: PWM buck dc-dc converter



LC filter corner frequency

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$


$$f_o > BW_{tracking}$$

Filtered output voltage


$$v_{dd}(t) \approx d(t)V_{in}$$

Switching frequency requirement

$$f_s \gg BW_{tracking}$$

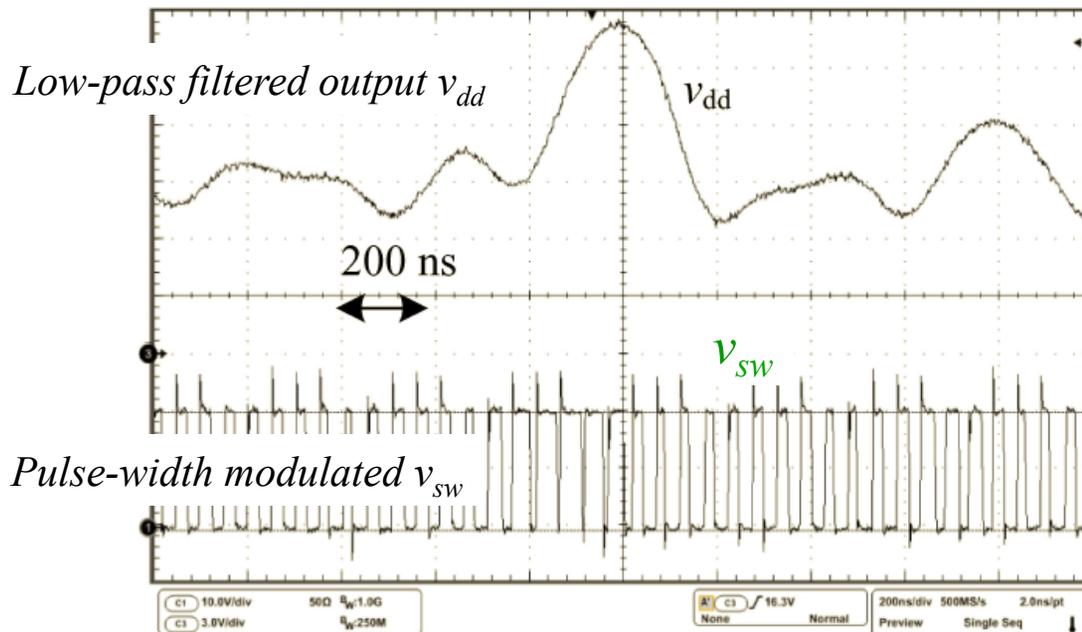

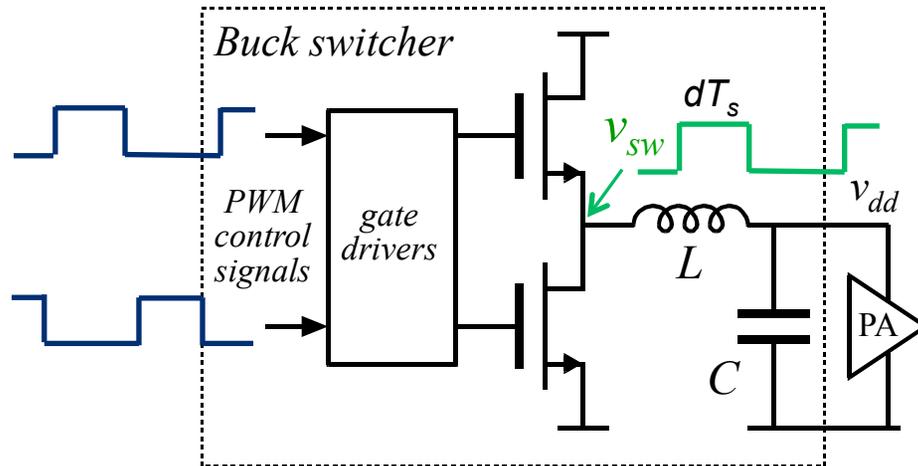CU CoPEC **Challenge: high-efficiency at high switching frequency**



LC filter corner frequency

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$f_o > BW_{tracking}$$

Filtered output voltage


$$v_{dd}(t) \approx d(t)V_{in}$$


Switching frequency requirement

$$f_s \gg BW_{tracking}$$



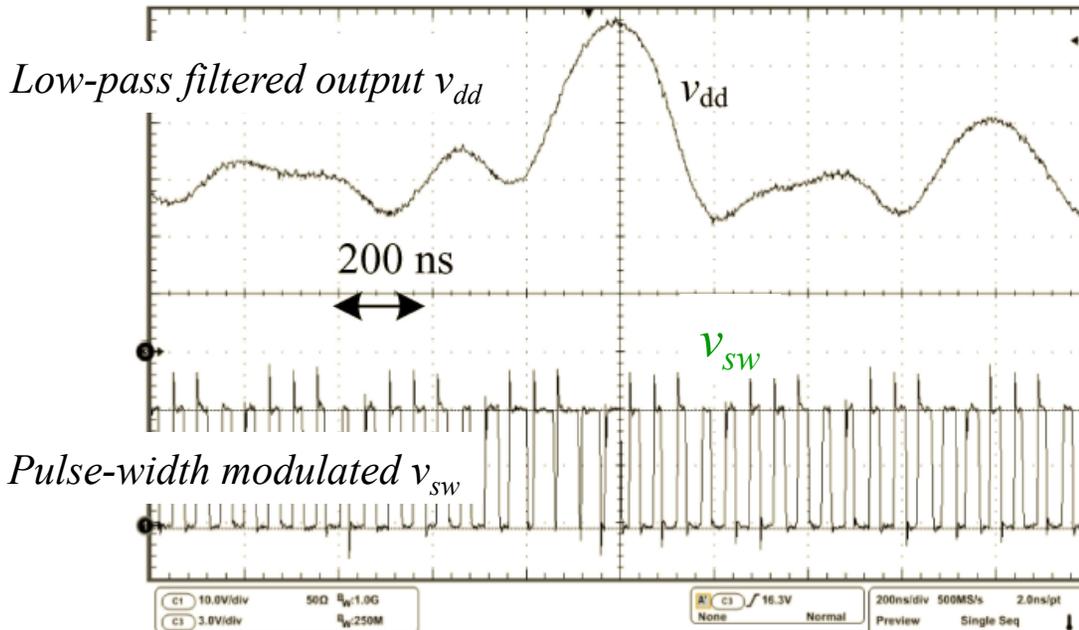*Conventional switched-mode power converter designs are limited to low switching frequencies (MHz) due to switching losses proportional to  $f_s$*



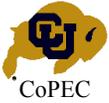


# Approach: monolithic VHF GaN switchers

---

## Switched-mode converter design techniques in GaN process

- Gate-drive integration
  - Enables efficient PWM of high-bridge power stage at VHF
  - Enables logic-level inputs to monolithic GaN switcher chip
- Zero-voltage switching
  - Reduces switching losses
- Multi-phase conversion
  - Improves tracking bandwidth to switching frequency ratio
  - Enables power scaling
  - Reduces ripple
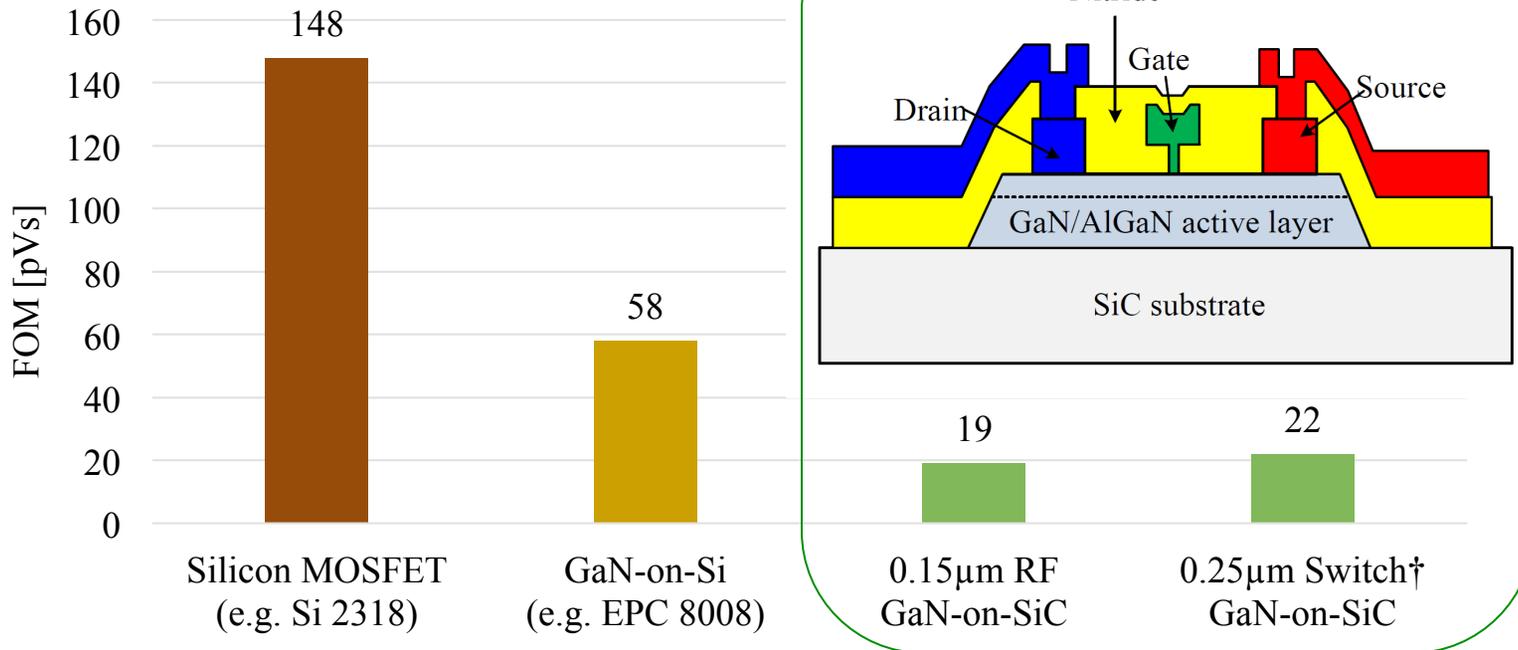
# GaN-on-SiC process: switch FOM = $R_{on,s}Q_{g,s}$




Superior figure of merit allows switched-mode converter circuit design techniques leading to high efficiencies at very high switching frequencies


Integrated converter circuits tested at 10-400 MHz switching frequencies, up to 20V in the 0.15µm RF process, and up to 50V in the 0.25µm Switch process

NMOS-only process: circuit design challenges
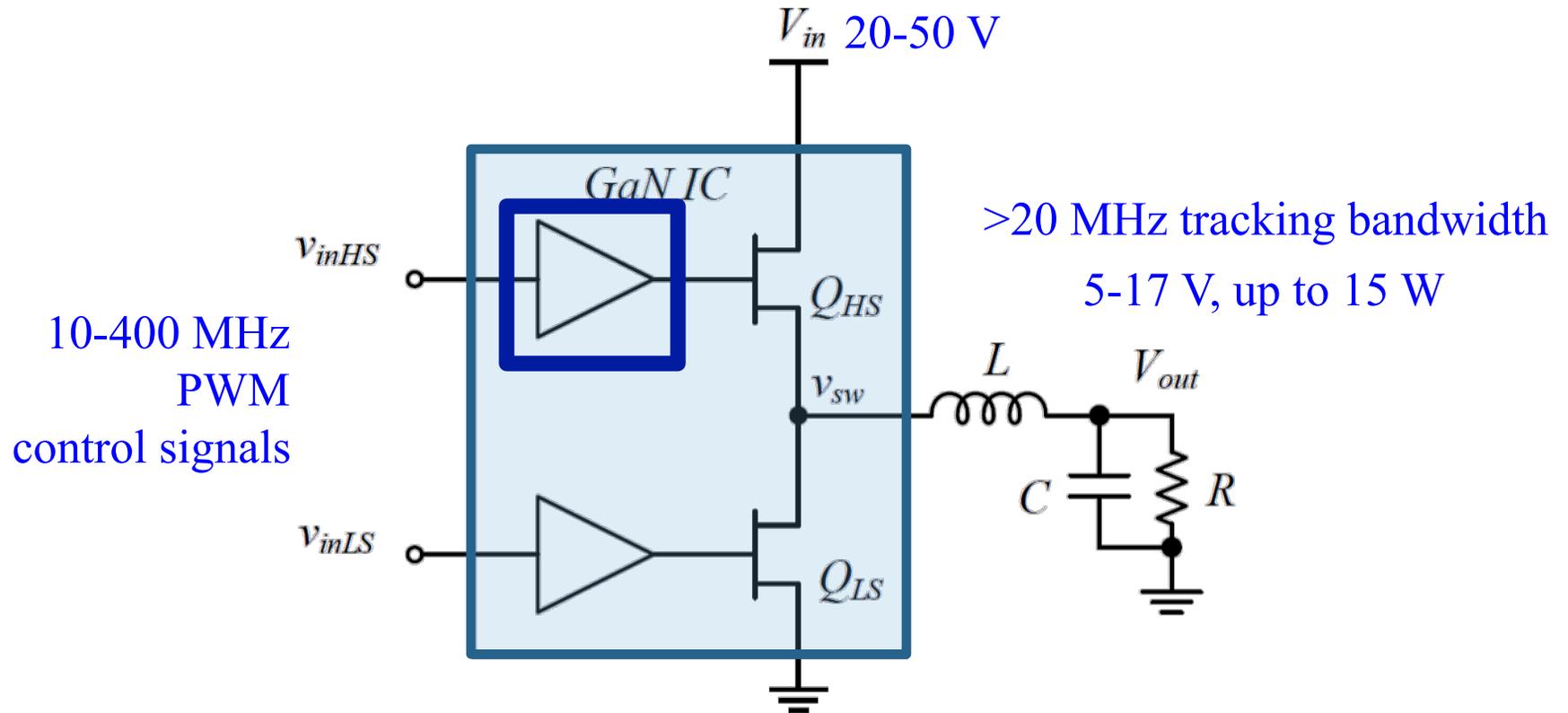
# 10-400 MHz Integrated GaN PWM Buck Converters



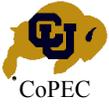*Key circuit innovation: level-shifting high-side gate driver in GaN-on-SiC process to support very high frequency PWM control*





# Integrated Gate Drivers for Half-Bridge Power Stage

---

- Active pull-up driver
- Bootstrap drive
- Modified active pull-up driver

# Active pull-up driver

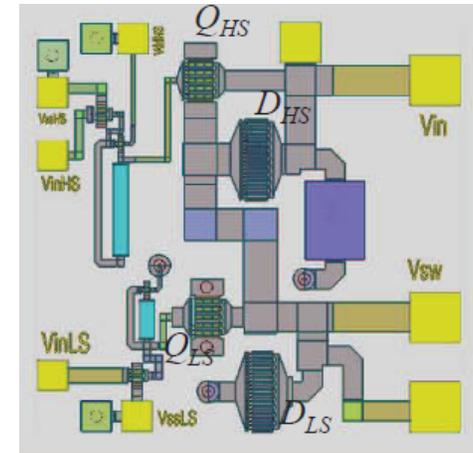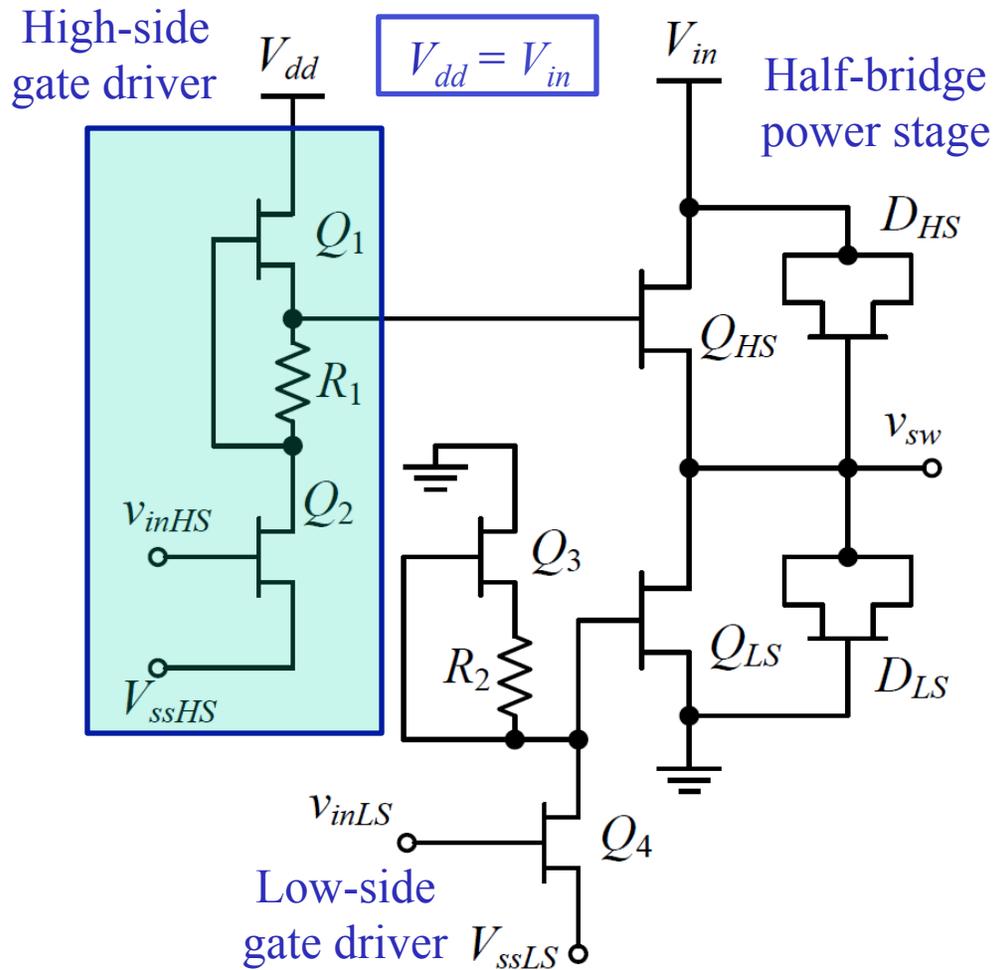

Chip layout:  $2.4 \times 2.3 \text{ mm}$

Half-bridge power stage  
 $Q_{HS}/D_{HS}$ ,  $Q_{LS}/D_{LS}$

High-side gate driver  
 $Q_1$ ,  $R_1$ ,  $Q_2$


Low-side gate driver  
 $Q_3$ ,  $R_2$ ,  $Q_4$

$Q_{HS}$ , $Q_{LS}$	$D_{HS}$ , $D_{LS}$	$Q_1$ , $Q_3$	$Q_2$ , $Q_4$	$R_1$	$R_2$
10x125 $\mu\text{m}$	10x120 $\mu\text{m}$	2x25 $\mu\text{m}$	4x50 $\mu\text{m}$	300 $\Omega$	125 $\Omega$

# Active pull-up driver operation




$Q_{HS}$  on,  $Q_{LS}$  off

$$I_{Q3} = 13.2 \text{ mA}$$

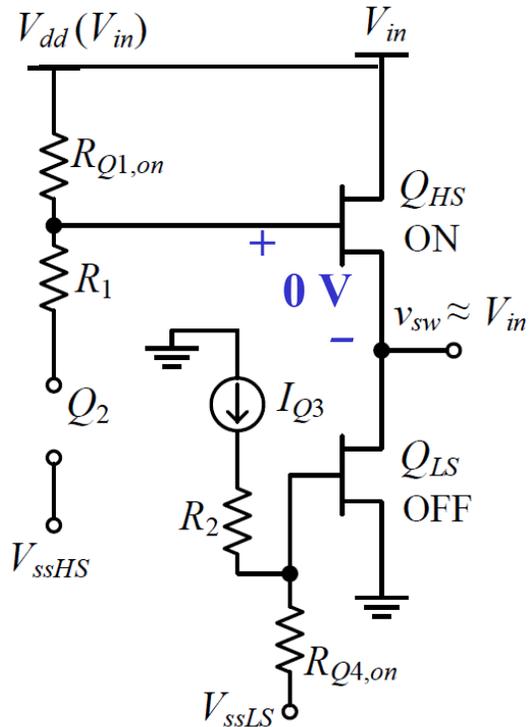

$Q_{HS}$  off,  $Q_{LS}$  on



$$I_{Q1} = 8.5 \text{ mA}$$

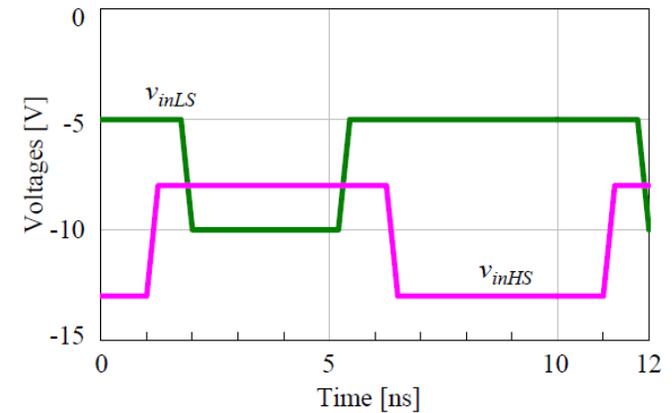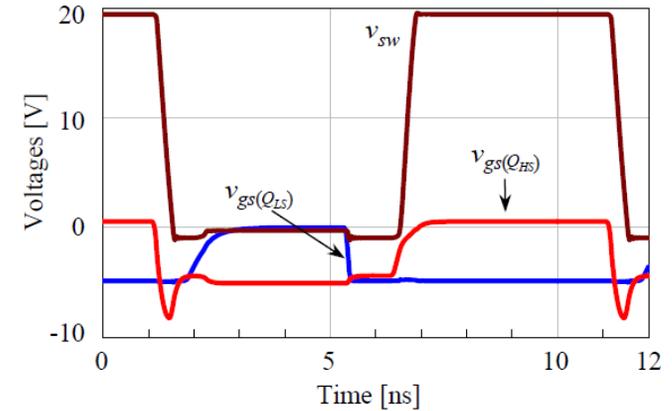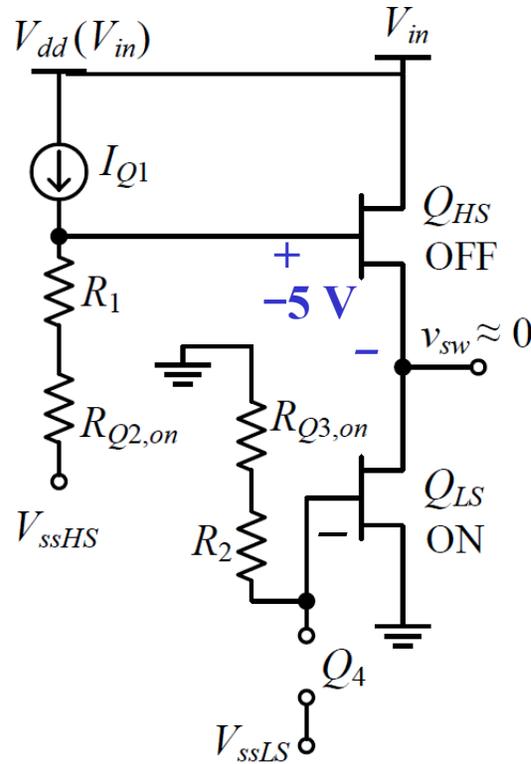

$$P_{d,conduction} = -DV_{ssLS}I_{Q3} + (1-D)(V_{in} - V_{ssHS})I_{Q1} \text{ HIGH}$$

$$D=0.5, I_o=0.25 \text{ A}$$

# Bootstrap driver

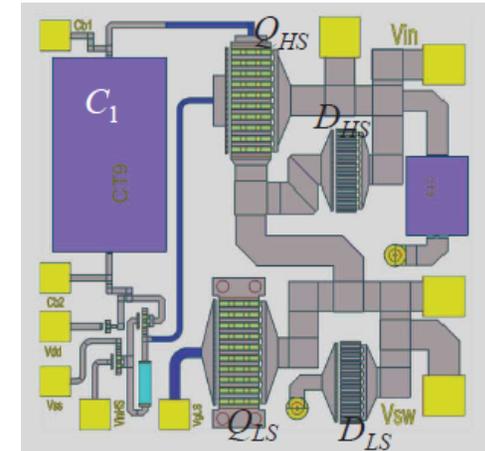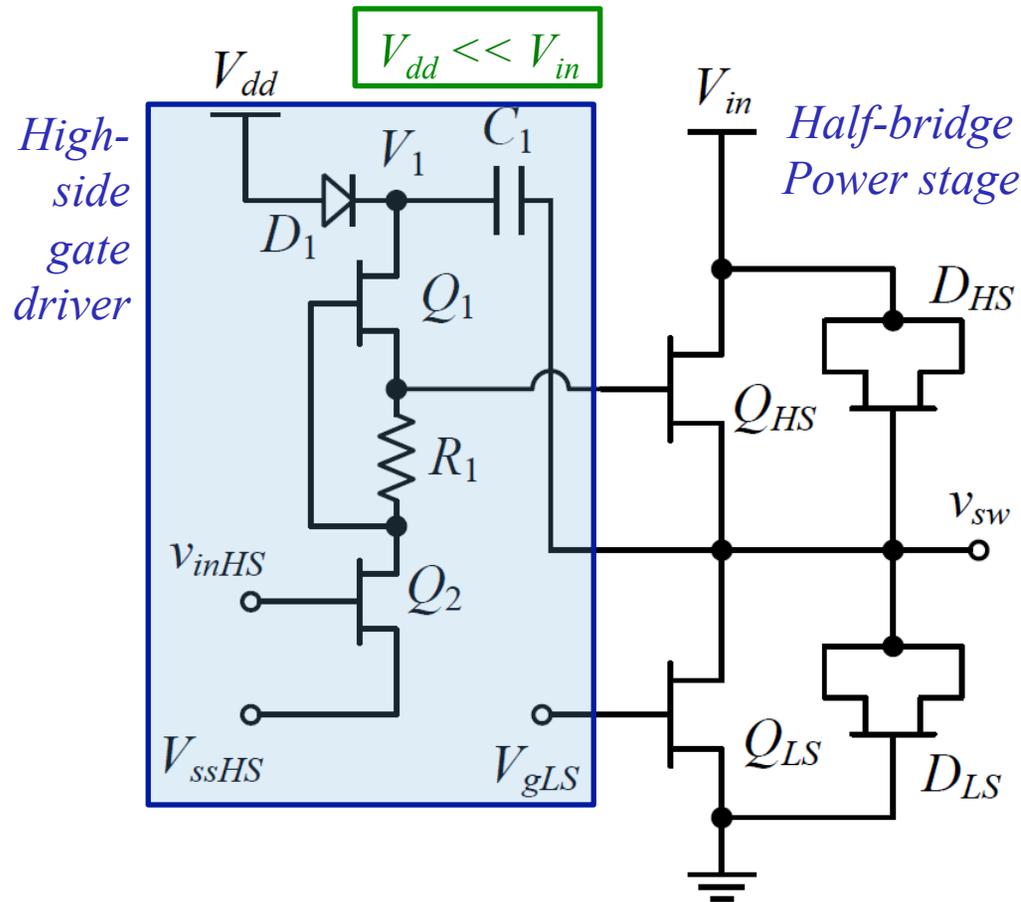

Chip layout:  $2.4 \times 2.3$  mm

Half-bridge power stage

$Q_{HS}/D_{HS}$ ,  $Q_{LS}/D_{LS}$

High-side gate driver

$Q_1$ ,  $R_1$ ,  $Q_2$ ,  $D_1$ ,  $C_1$


Low-side gate driver

$Q_3$ ,  $R_2$ ,  $Q_4$

$Q_{HS}$ , $Q_{LS}$	$D_{HS}$ , $D_{LS}$	$Q_1$ , $Q_2$	$D_1$	$C_1$	$R_1$
20x200 $\mu$ m	20x100 $\mu$ m	4x25 $\mu$ m	2x25 $\mu$ m	126 pF	175 $\Omega$



# Bootstrap driver operation

$Q_{HS}$  on,  $Q_{LS}$  off

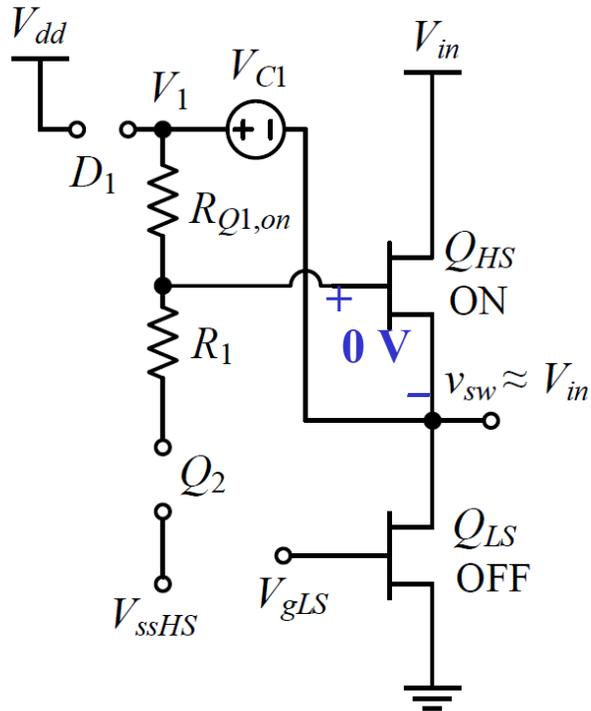

$Q_{HS}$  off,  $Q_{LS}$  on

$$I_{Q1} = 13.5 \text{ mA}$$

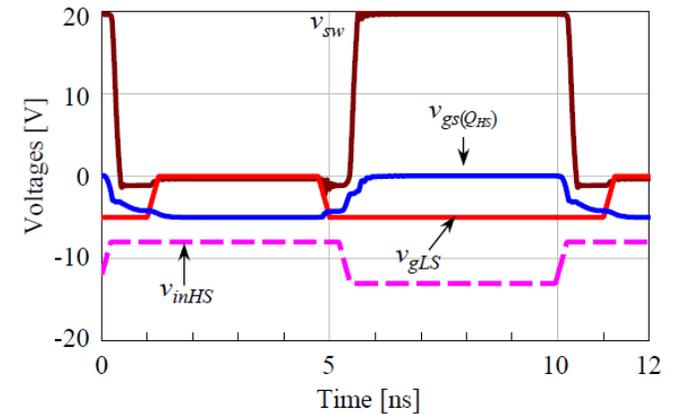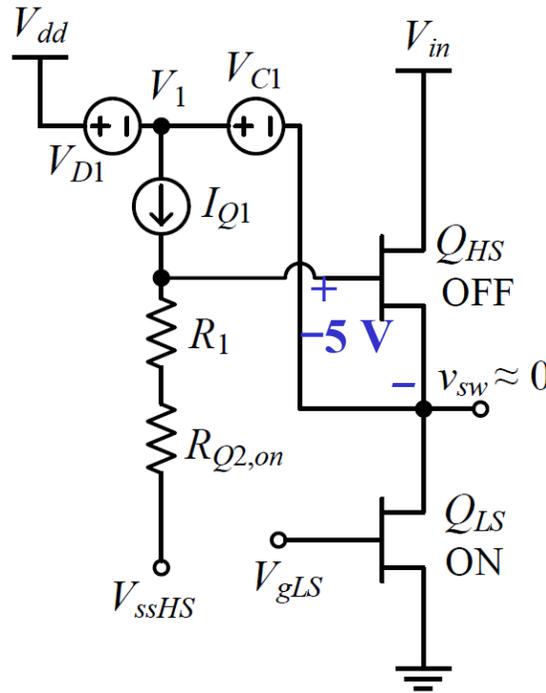

$$D=0.5, I_o=0.25 \text{ A}$$



$$P_{d,conduction} = -DV_{ssLS}I_{Q3} + (1-D)(-V_{ssHS})I_{Q1}$$

LOW

Low driver power loss,

but a bootstrap capacitor is required (large chip area, or external)

# Modified active pull-up driver

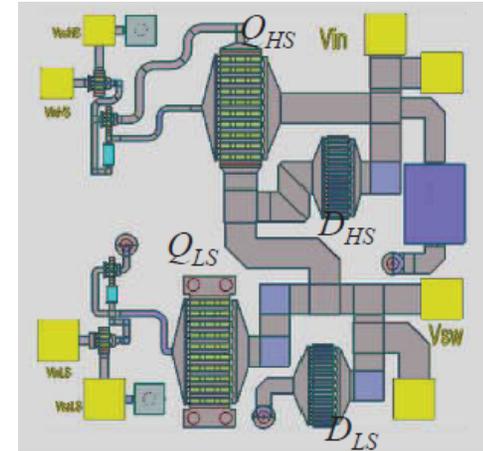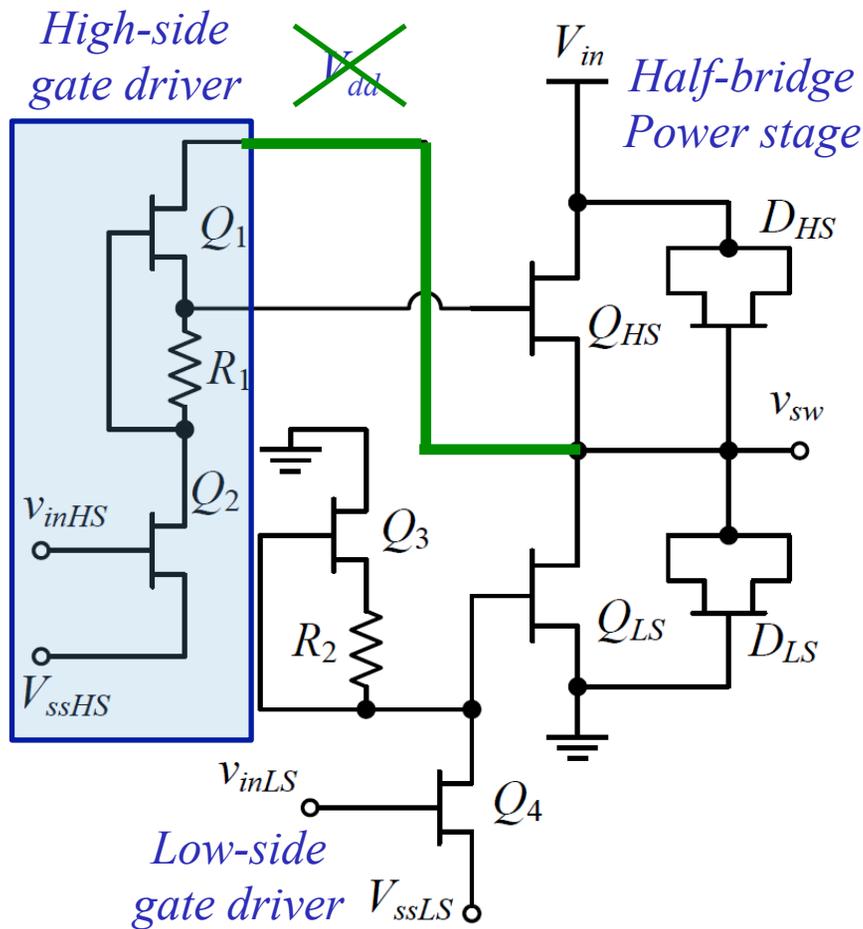

Chip layout:  $2.4 \times 2.3$  mm

Half-bridge power stage  
 $Q_{HS}/D_{HS}$ ,  $Q_{LS}/D_{LS}$

Half-side gate driver  
 $Q_1$ ,  $R_1$ ,  $Q_2$


Low-side gate driver  
 $Q_3$ ,  $R_2$ ,  $Q_4$

$Q_{HS}$ , $Q_{LS}$	$D_{HS}$ , $D_{LS}$	$Q_1$ , $Q_3$	$Q_2$ , $Q_4$	$R_1$	$R_2$
20x200 $\mu$ m	20x100 $\mu$ m	4x25 $\mu$ m	4x50 $\mu$ m	100 $\Omega$	75 $\Omega$

# Modified active pull-up driver operation




$Q_{HS}$  on,  $Q_{LS}$  off

$$I_{Q3} = 25.6 \text{ mA}$$

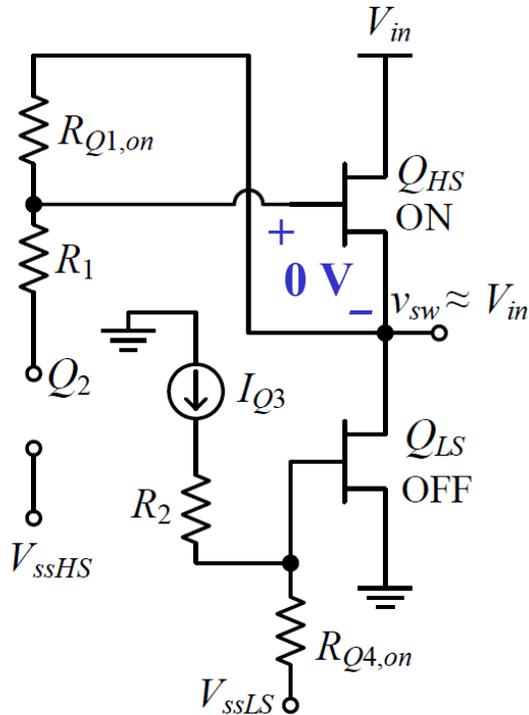

$Q_{HS}$  off,  $Q_{LS}$  on

$$I_{Q1} = 23.3 \text{ mA}$$

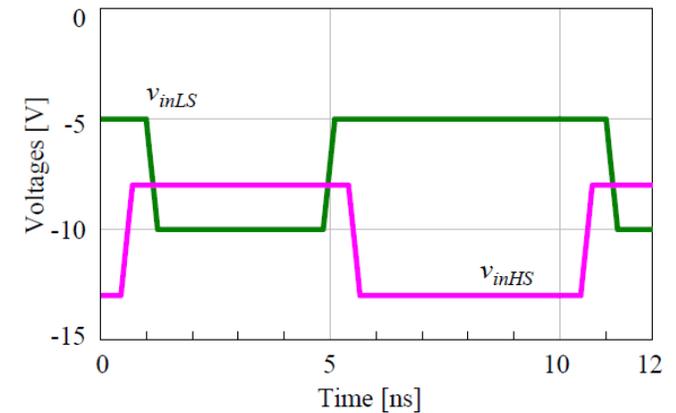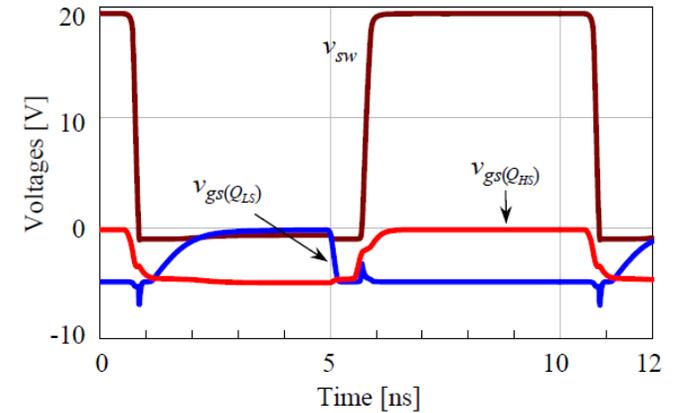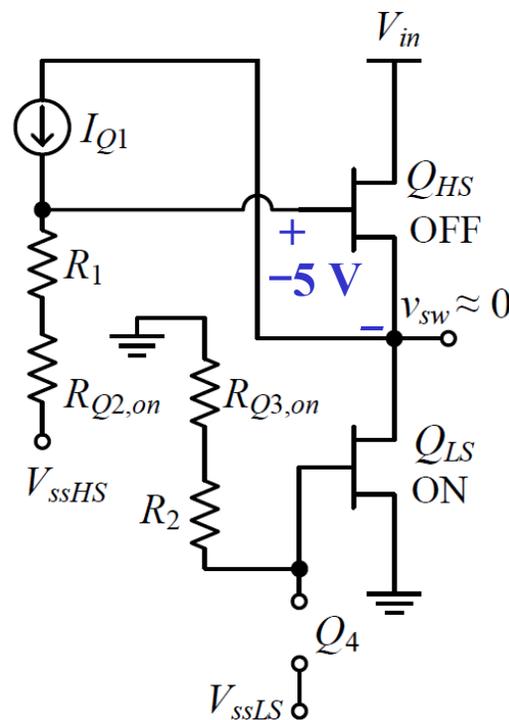


$$D = 0.5, I_o = 0.25 \text{ A}$$

$$P_{d,conduction} = -DV_{ssLS}I_{Q3} + (1-D)(-V_{ssHS})I_{Q1}$$


LOW

Low driver power loss, and no bootstrap capacitor required

# Zero-voltage-switching (ZVS) operation

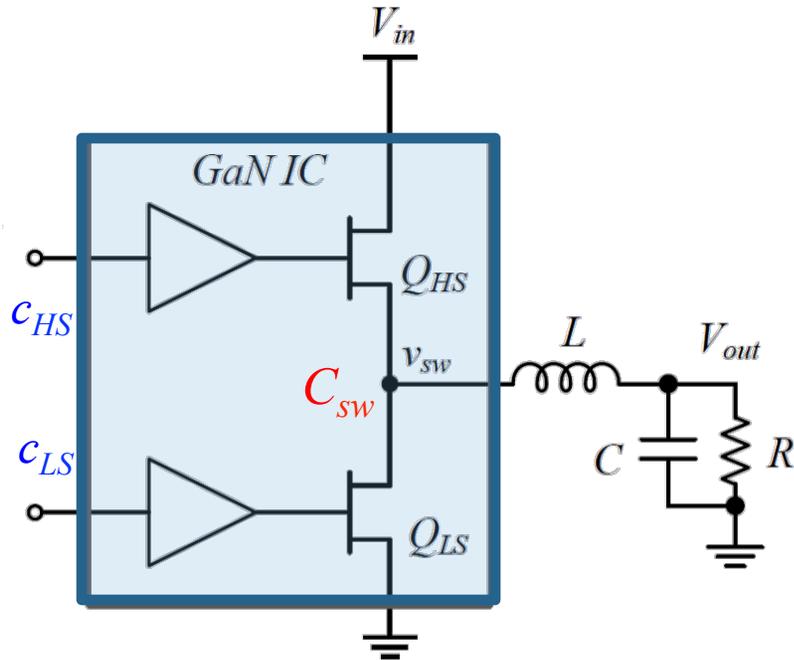


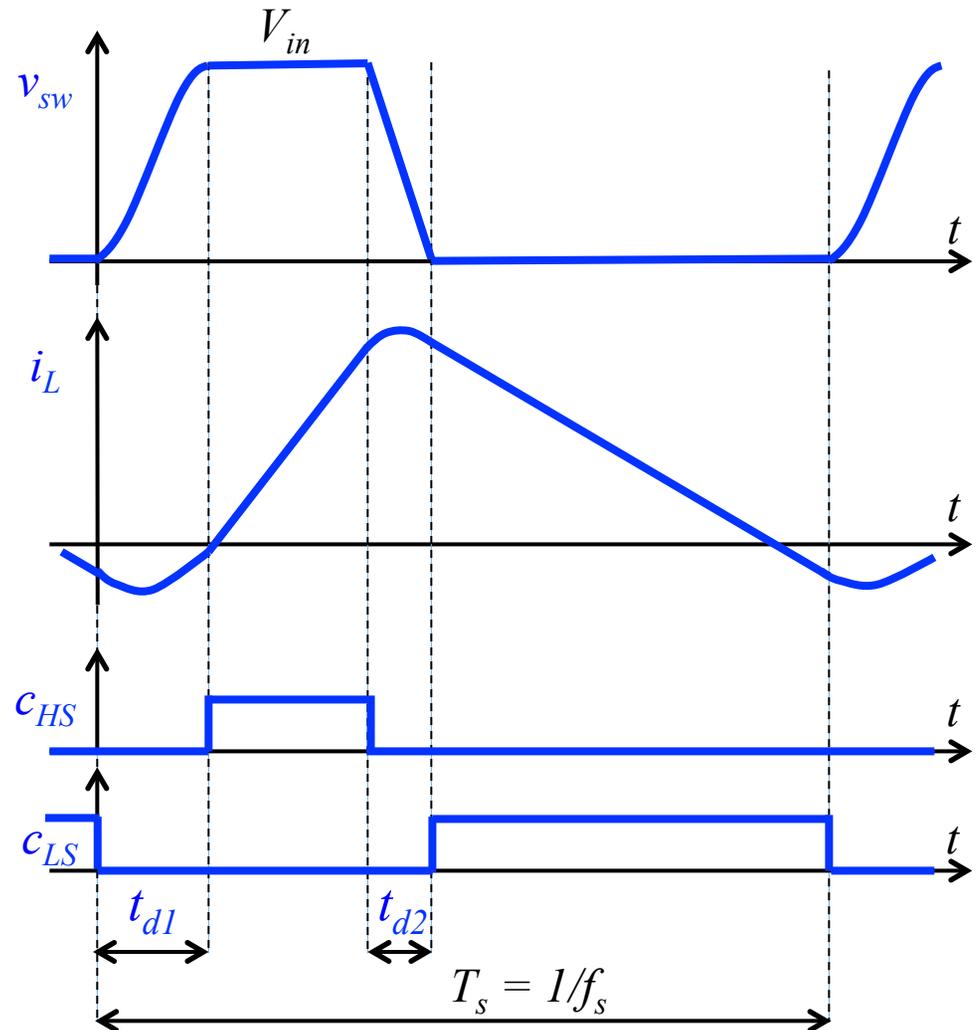- $L$ - $C_{sw}$  resonant ZVS transitions
- Much reduced switching losses
- Dynamically adjusted dead-times  $t_{d1}$ ,  $t_{d2}$ , with around 100ps resolution




# Experimental results


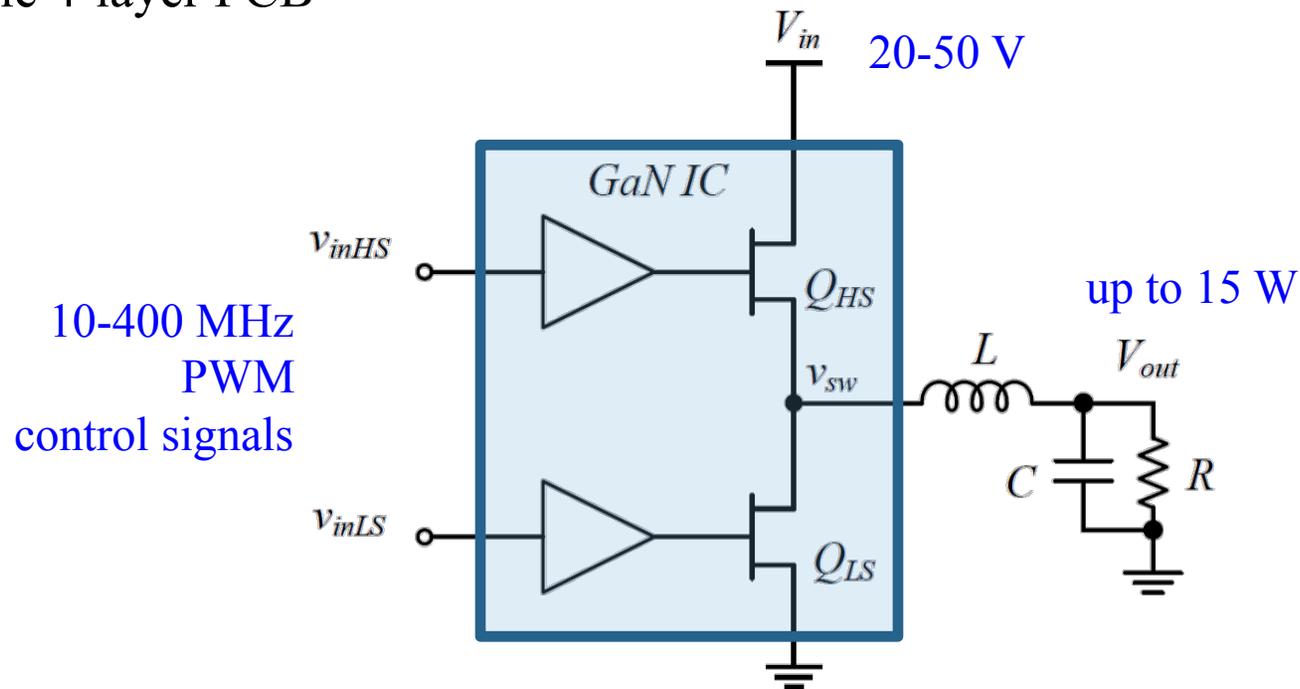
- 10-400 MHz PWM switching, mostly ZVS operation
- Control: Altera Stratix IV FPGA, 125 ps resolution
- Chips packaged in: 20-pin 4x4mm QFN package
- Filter components
  - Low-ESR capacitors (ATC)
  - High- $Q$  air-core inductors (Coilcraft), 10-400 nH
- Simple 4-layer PCB






# Switching waveforms

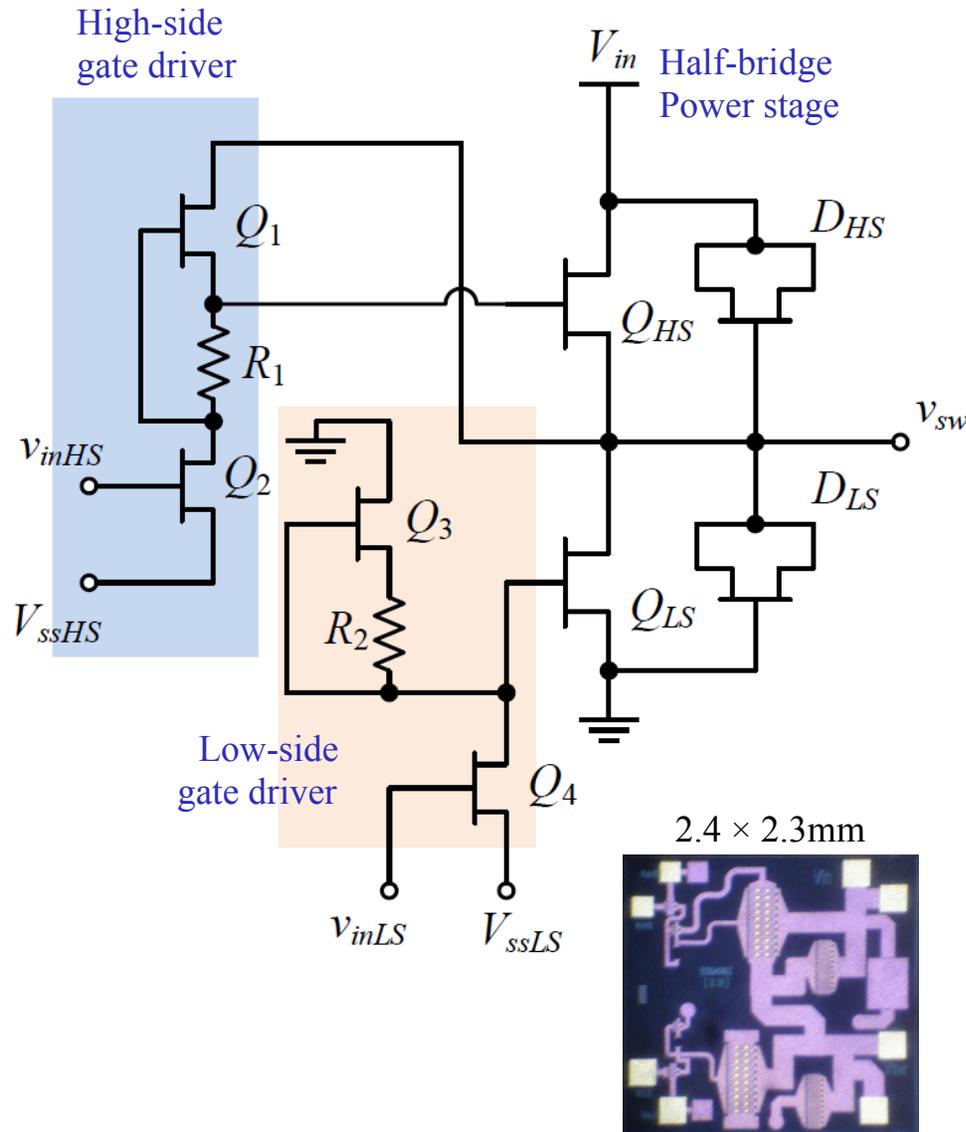

100 MHz switching waveforms

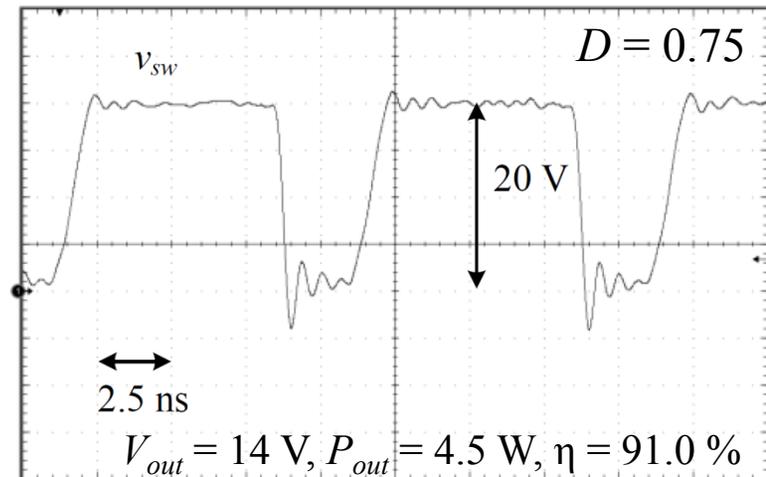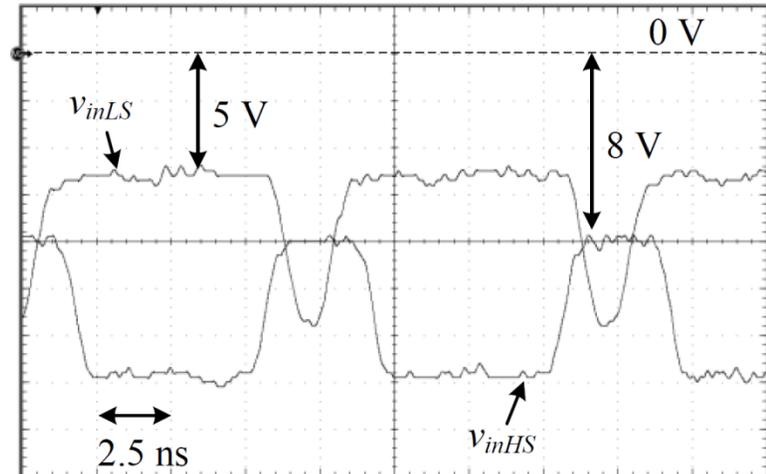

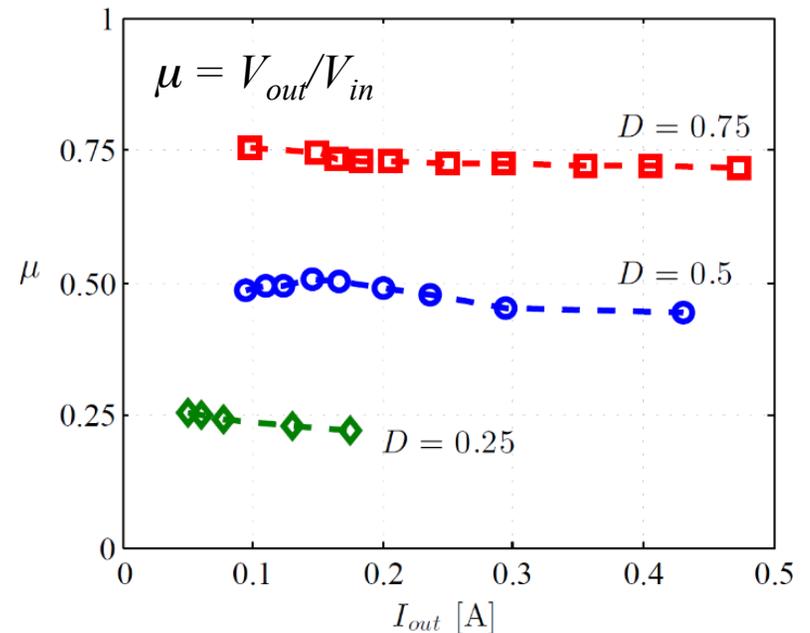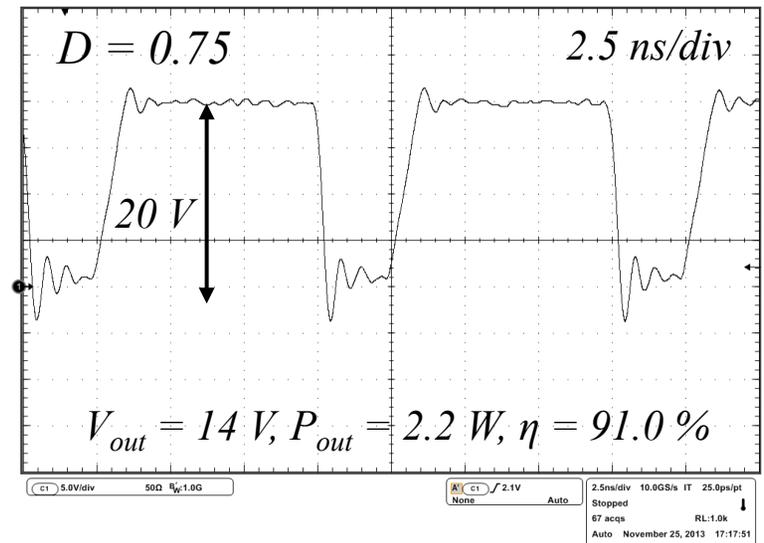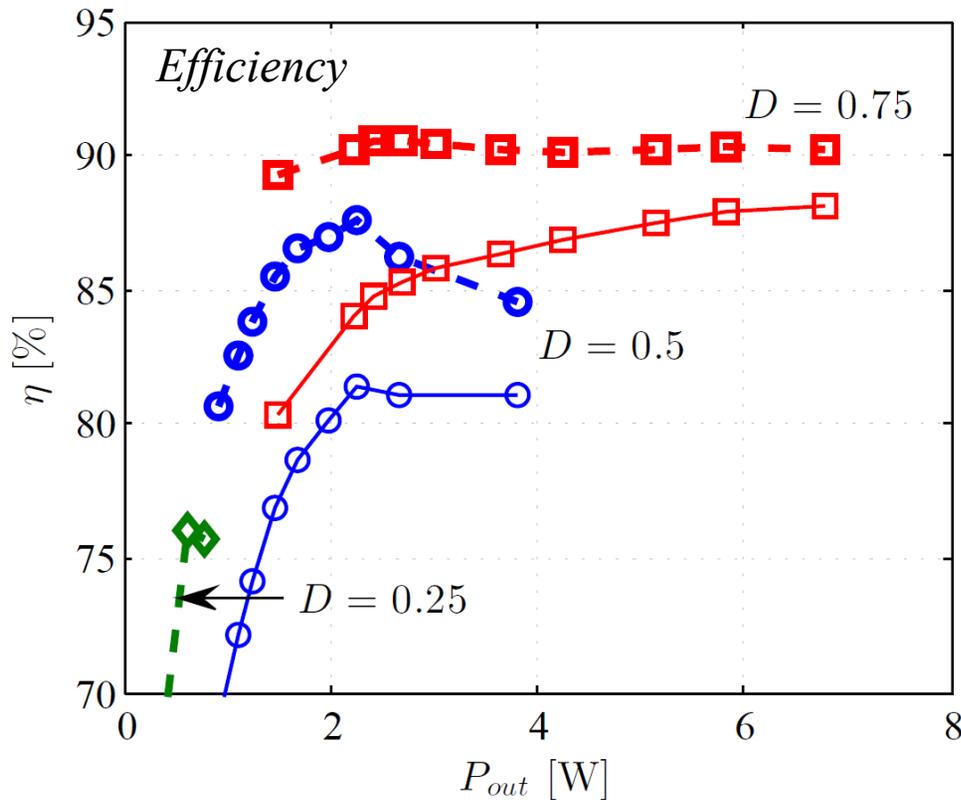
# Experimental results: 100 MHz switching




- 100 MHz switching
- $P_{out}$  up to 7 W
- 91% peak power-stage efficiency
- $< 0.2 \text{ W}$  driver loss
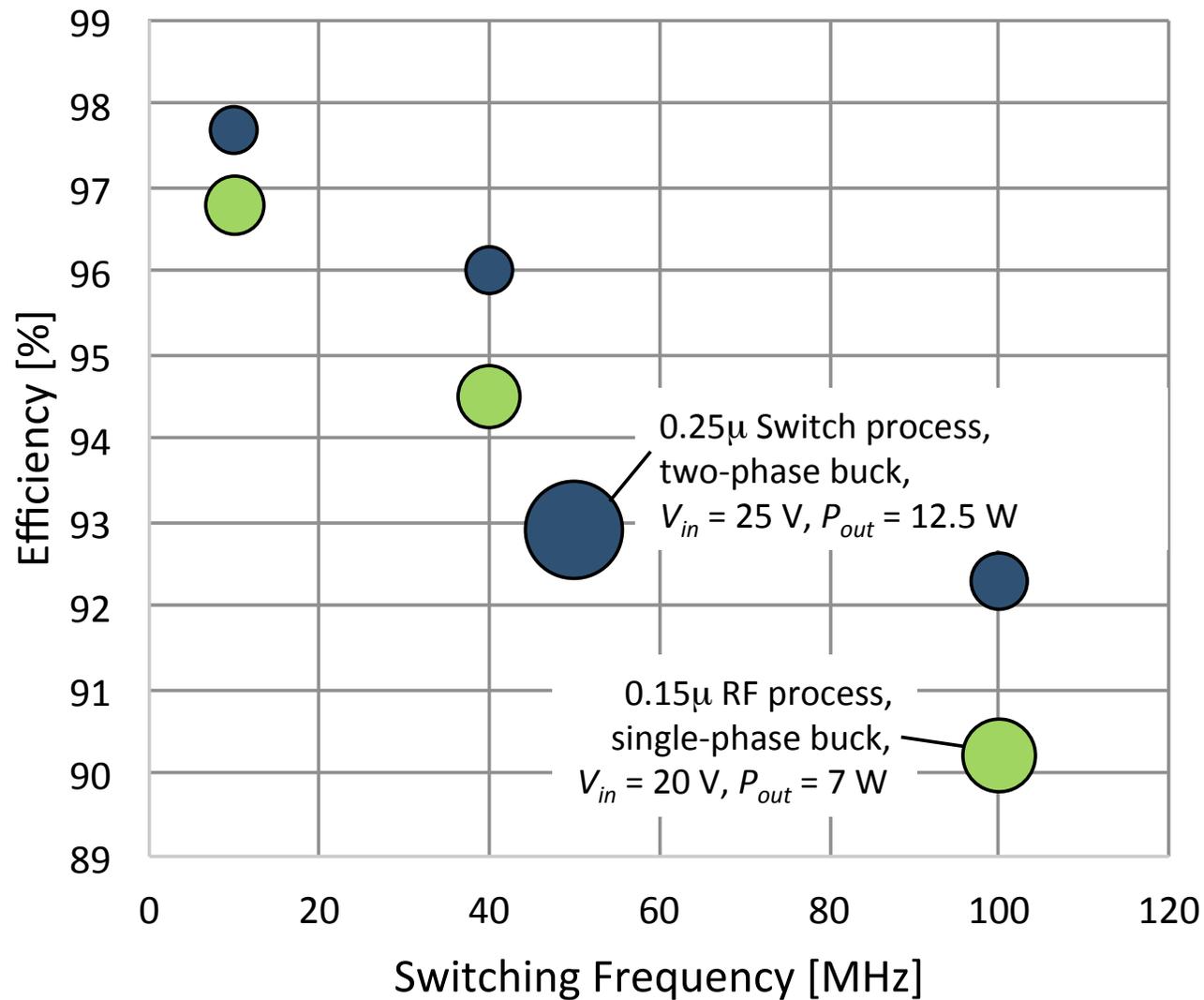
# Monolithic GaN switchers: efficiency versus sw. frequency



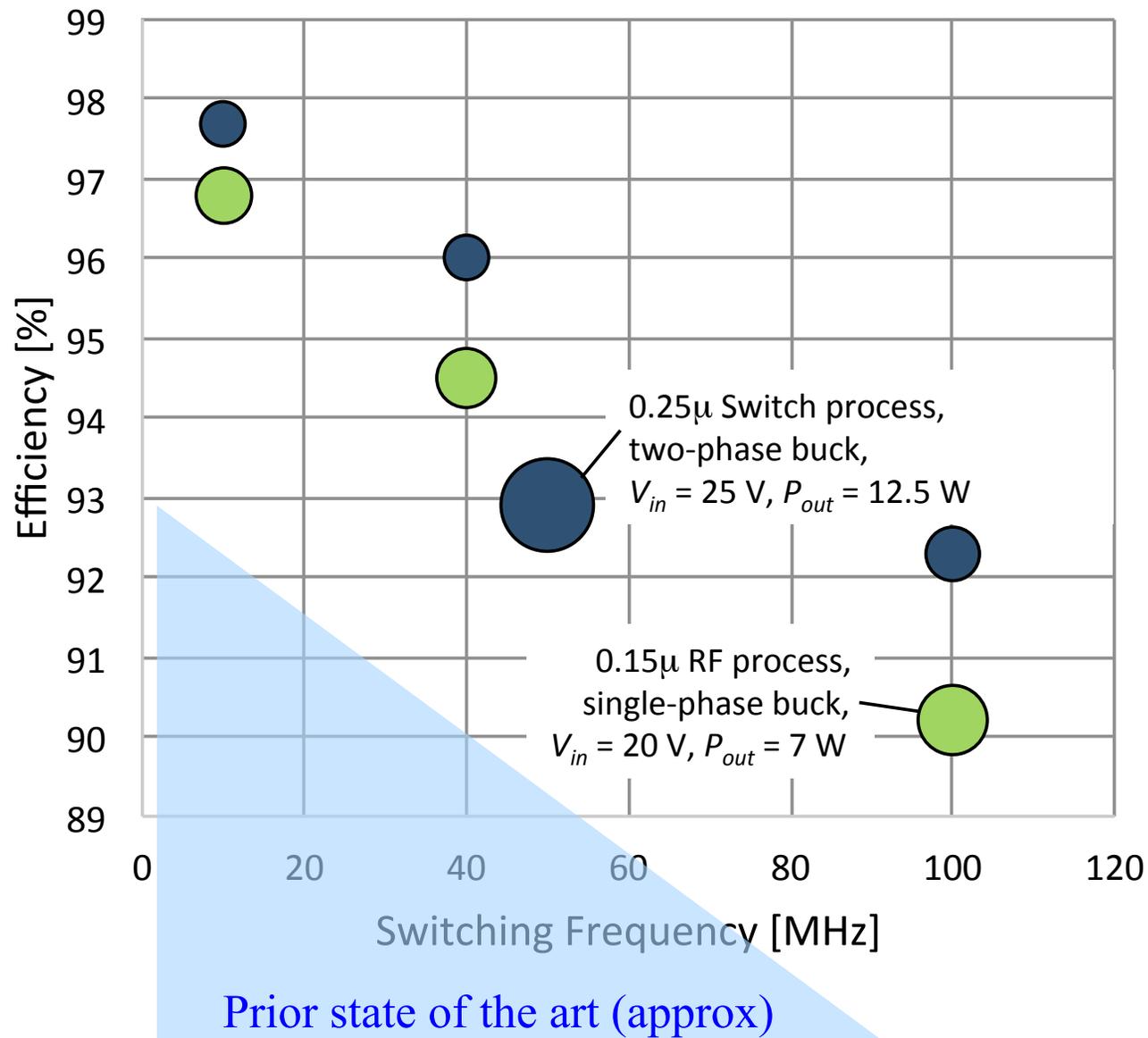
# Monolithic GaN switchers: efficiency versus sw. frequency




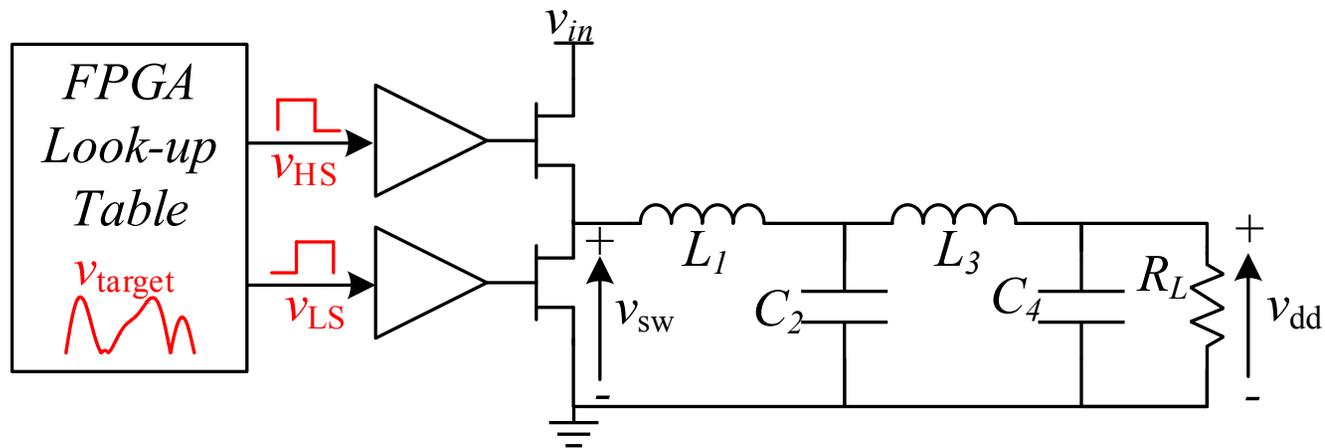
# Application: envelope tracking supply for RFPAs

- Target signal: 20 MHz bandwidth LTE envelope
- 4<sup>th</sup> order filter, 25 MHz cut-off frequency
- 100 MHz switching frequency





$L_1$	$C_2$	$L_3$	$C_4$	$R_L$	$V_{in}$	$P_{out,pk}$
28 nH	820 pF	307 nH	270 pF	30 $\Omega$	20 V	10 W

# Envelope tracking experimental results

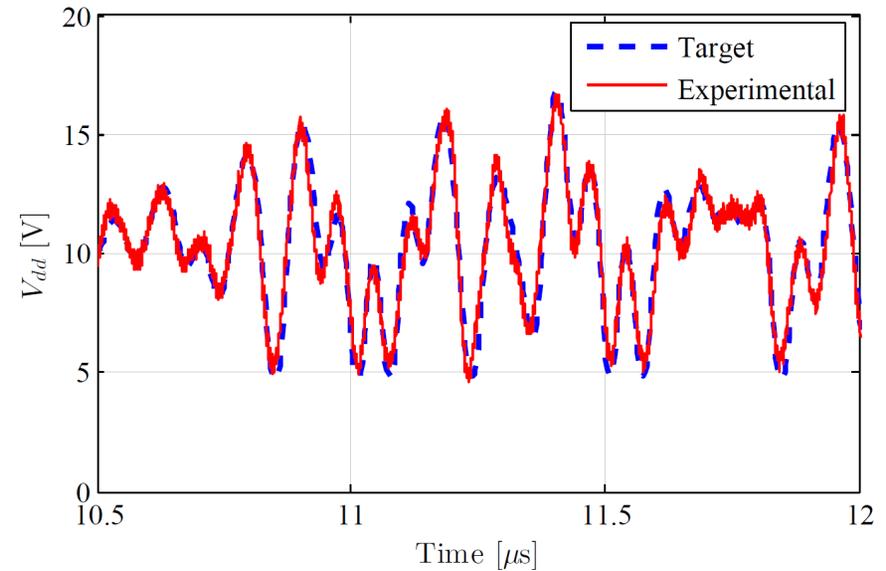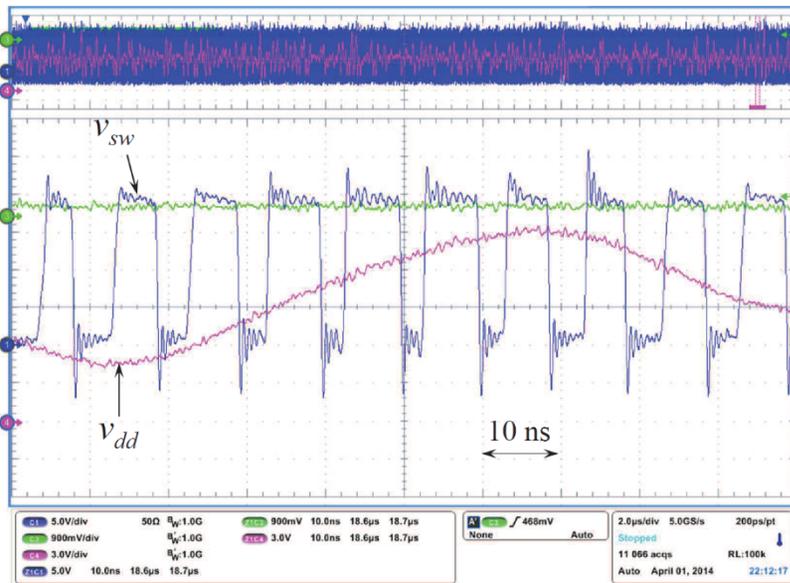

- 20 MHz LTE envelope, 100 MHz switching frequency
- Power stage efficiency: 83.7%
- Total efficiency: 80.1% (including on-chip driver loss)
- Normalized RMS error: 5.4%
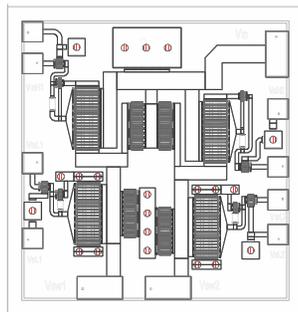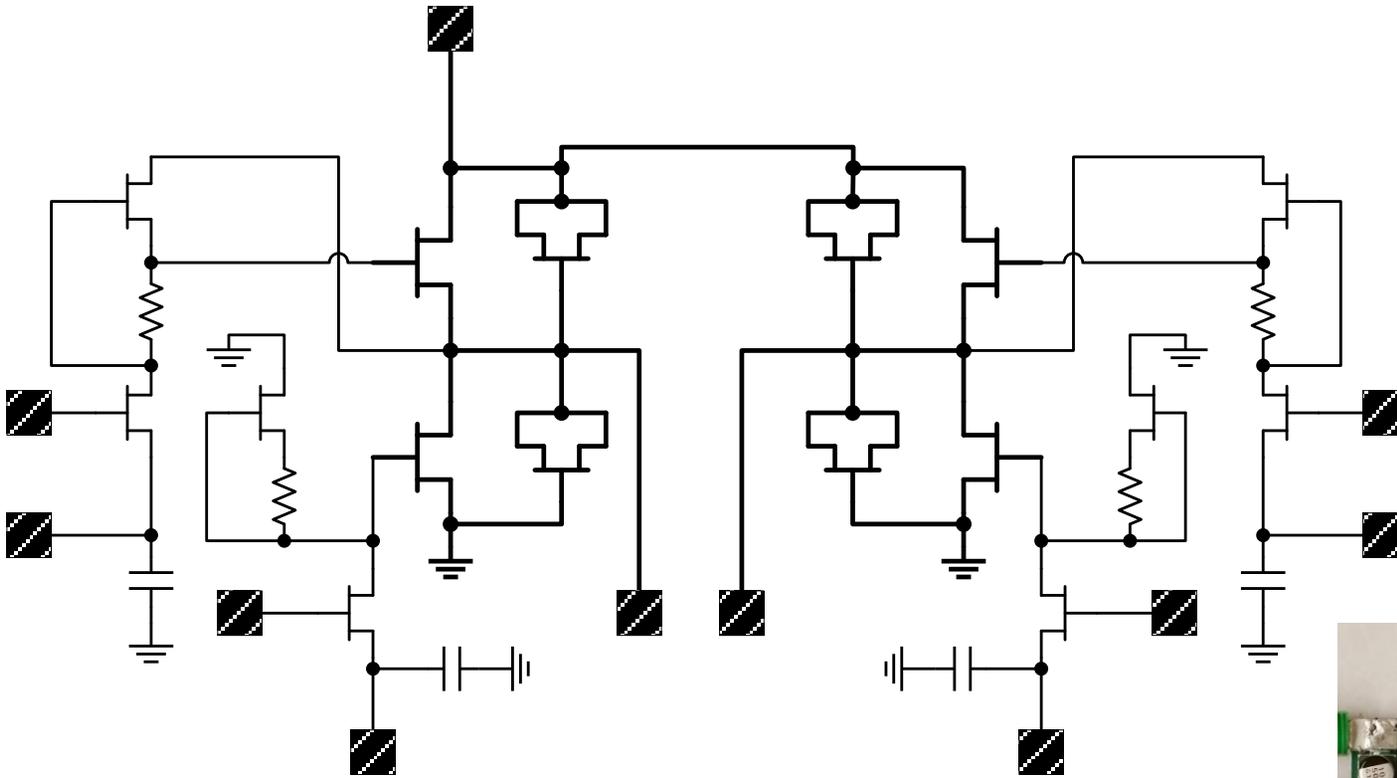
# Integrated two-phase GaN buck converter chip



2.6 x 2.7 mm

0.25 $\mu$  GaN-on-SiC  
switch process

20-pin QFN package


Air-core inductors




# Two-phase switching drain supply modulator

FOURTH-ORDER FILTER DESIGNS FOR TWO PHASE CONVERTERS.


BW	$L_1$	$C_2$	$L_3$	$C_4$	$f_{sw}$
5 MHz	538 nH	2.7 nF	1.5 $\mu$ H	1.2 nF	10 MHz
20 MHz	90 nH	680 pF	307 nH	200 pF	50 MHz

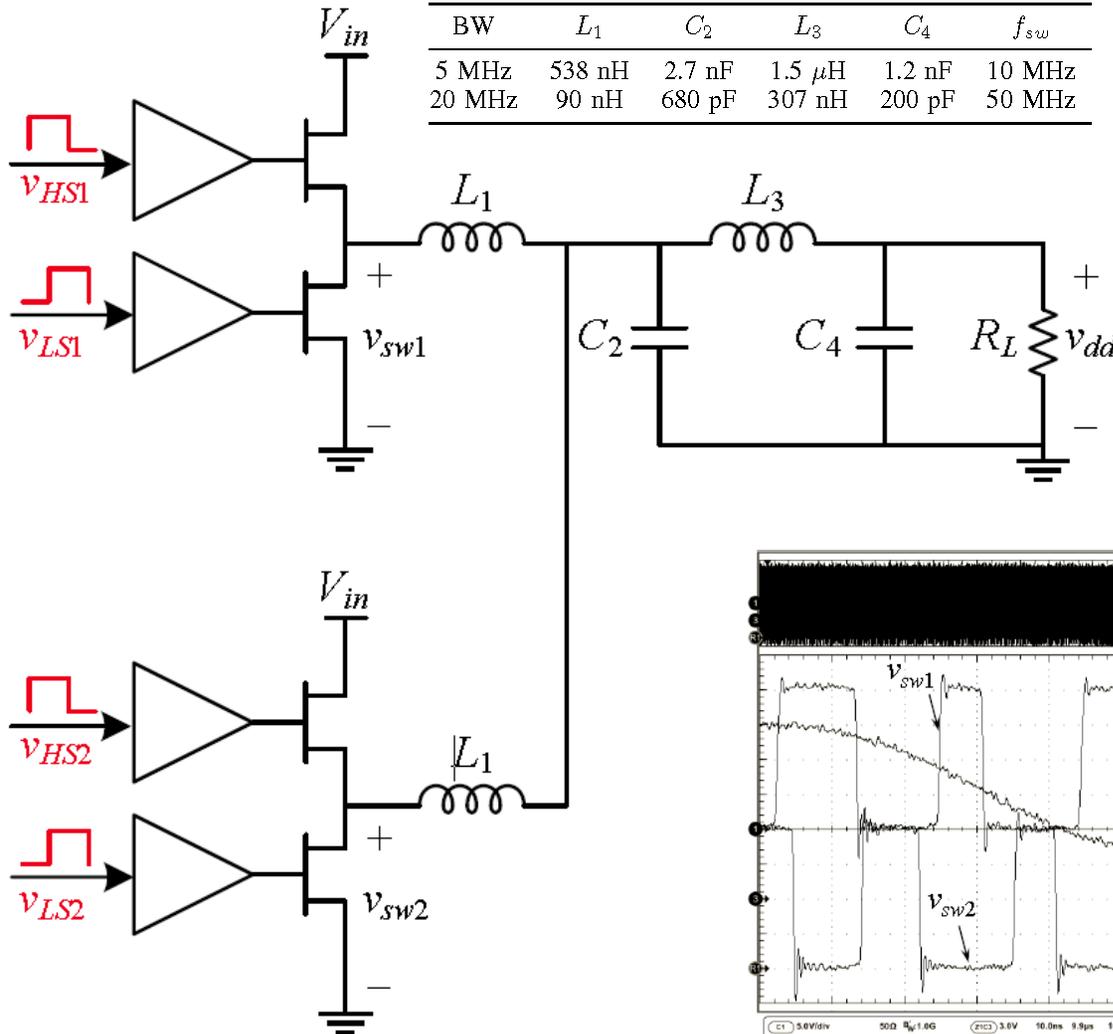

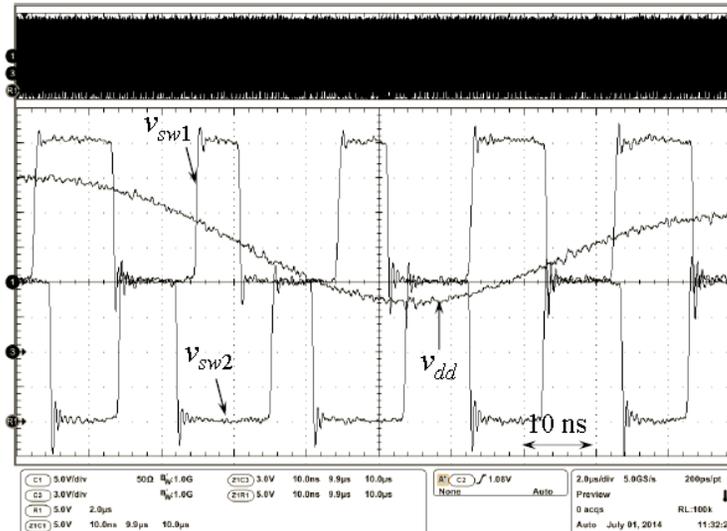- 50 MHz per-phase switching frequency
- 20 MHz tracking bandwidth
- 3.4% RMSE tracking 20MHz LTE envelope
- **93.2% peak, 85% total efficiency**



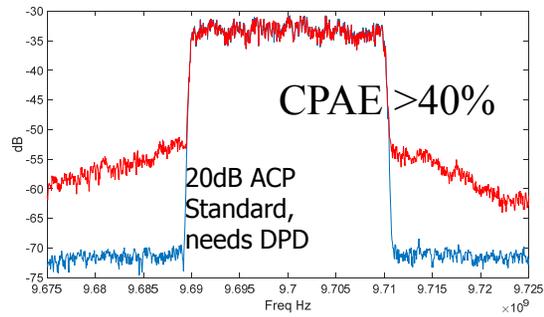
# System integration: monolithic high-efficiency RF PA




RF VHF/  
UHF  
input



X-band input

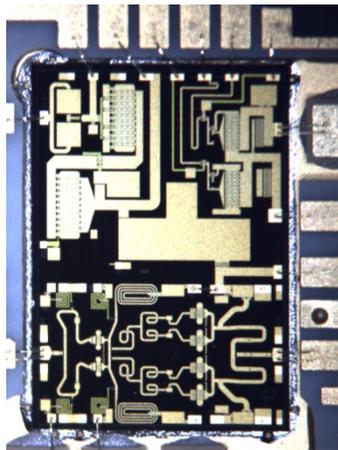


5.4 x 3.8 mm MMIC

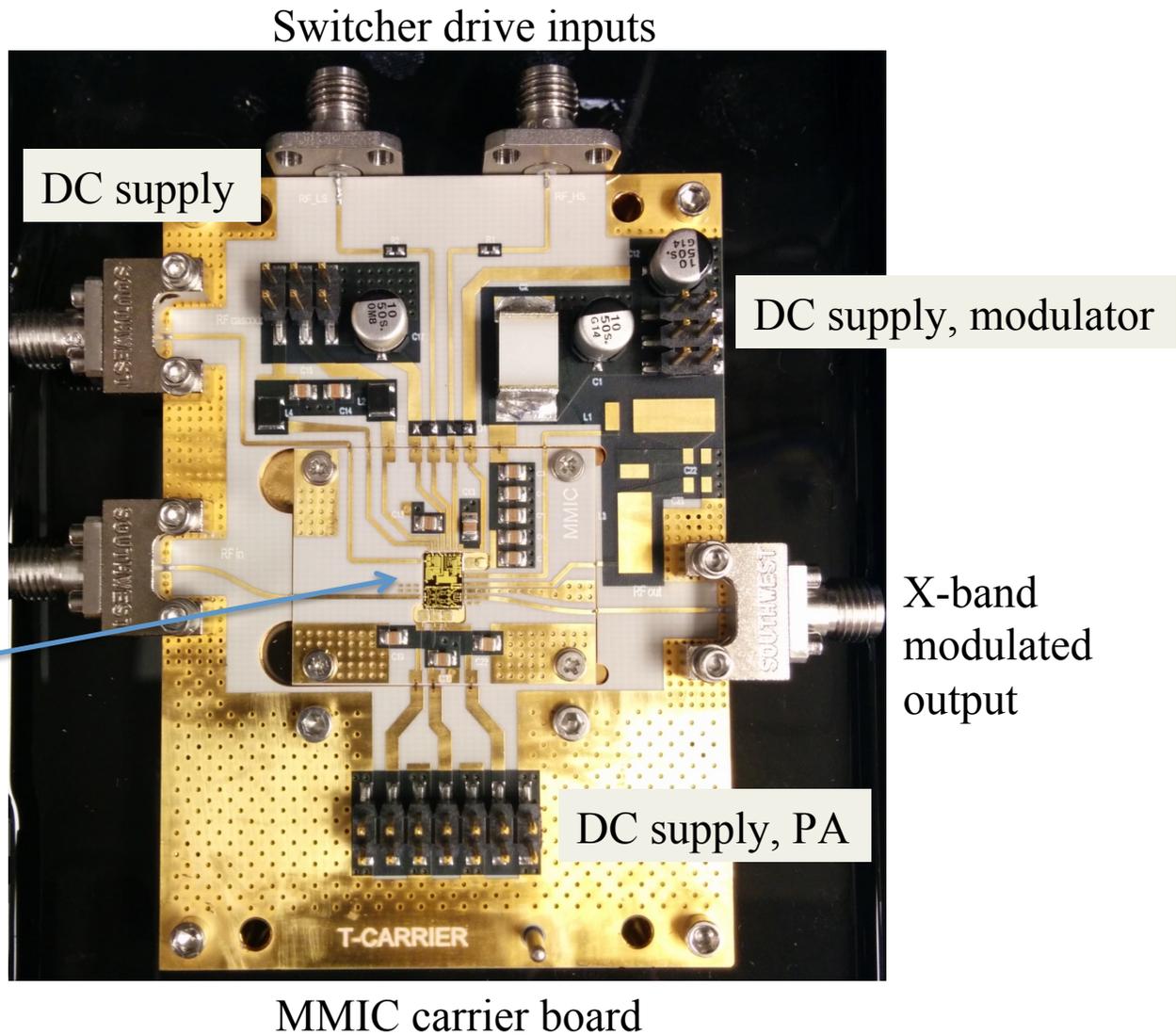
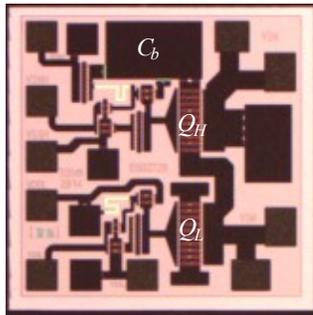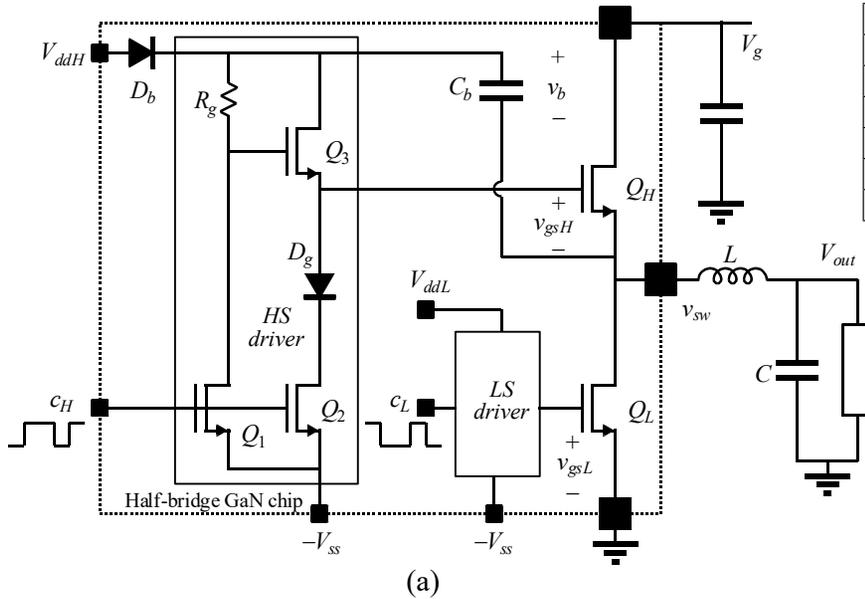
# Monolithic GaN switchers in an E-mode process






Switching frequency, $f_s$ [MHz]	20	50	100	200	400	100
Input voltage [V]	25	25	25	25	20	45
Maximum output power [W]	16.0	10.1	7.1	3.4	5.0	6.0
Peak power stage efficiency [%]	95.0	94.2	93.2	86.5	72.5	91.7
Peak total efficiency [%]	92.5	91.7	89.2	82.0	67.0	90.2
Inductance (L) [nH]	160	90	47	22	12.5	90
Duty cycle (D) [%]	75	75	75	75	50	50

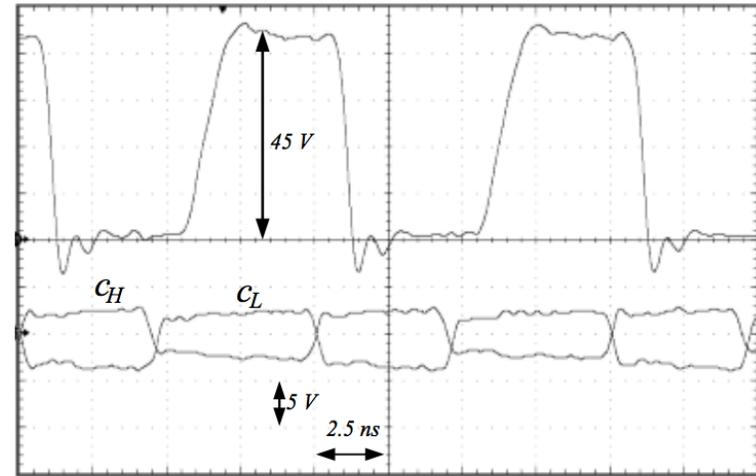

$$V_{out} = 23.1 \text{ V}, \quad P_{out} = 6 \text{ W}, \quad \eta = 91.7 \%$$

A.Sepahvand, Y.Zhang, D.Maksimovic, "High Efficiency 20-400 MHz PWM Converters using Air-Core Inductors and Monolithic Power Stages in a Normally-Off GaN Process," IEEE APEC 2016

# Scaling to higher power levels

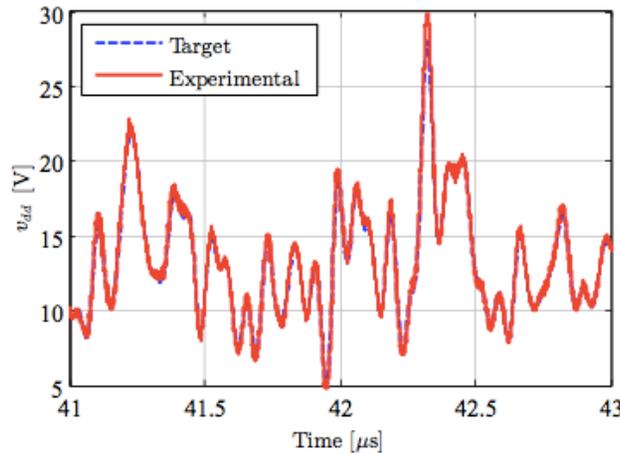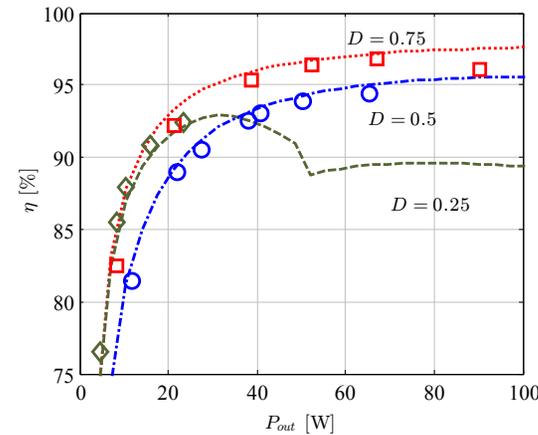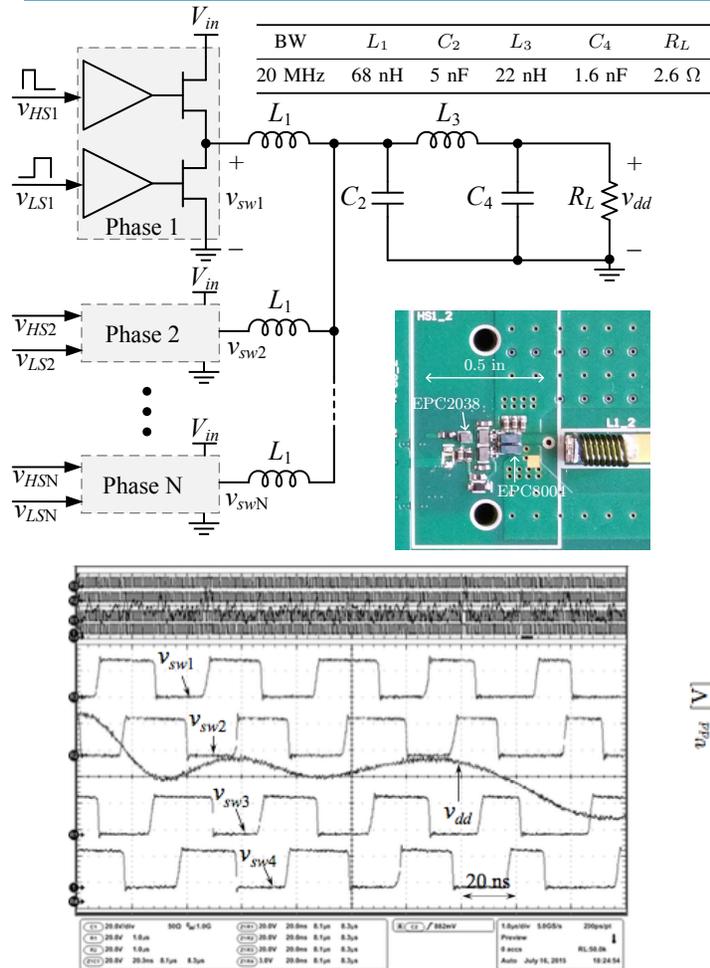

- 4-phase envelope tracker using EPC GaN fets
- Bootstrap driver with GaN fet synchronous bootstrap diode
- 25 MHz per-phase switching frequency
- 20 MHz tracking bandwidth for LTE signals
- 92.3% average efficiency at 67 W average output power

Y.Zhang, J.Strydom\*, M.Rooij\*, D.Maksimovic, “Envelope Tracking GaN Power Supply for 4G Cell Phone Base Stations,” IEEE APEC 2016. \*EPC



# Conclusions

---

- Wide bandgap semiconductor technologies open new opportunities in power electronics, but benefits of brute-force replacements of Si devices are limited
- Opportunities for innovations in power electronics
  - Converter circuit topologies and architectures
  - Magnetics
  - Soft switching
  - Control
  - Integration
  - Packaging
  - System architectures and system design

# Selected references: VHF GaN converters

---

- [1] J. Hoversten, S. Schafer, M. Roberg, M. Norris, D. Maksimovic, Z. Popovic, “Co-design of PA, Supply and Signal Processing for Linear Supply-Modulated RF Transmitters,” *IEEE Trans. Microwave Theory and Techniques, Special Issue on PAs*, pp. 210-220, April 2012.
- [2] M. Rodriguez, Y. Zhang, and D. Maksimovic, “High-frequency PWM buck converters using GaN-on-SiC HEMTs,” *IEEE Trans. Power Electron.*, vol. 29, no. 5, pp. 2462–2473, 2014.
- [3] Y. Zhang, M. Rodriguez, and D. Maksimovic, “High-frequency integrated gate drivers for half-bridge GaN power stage,” in *Control and Modeling for Power Electron.*, IEEE COMPEL 2014
- [4] Y. Zhang, M. Rodriguez, and D. Maksimovic, “100 MHz, 20 V, 90% efficient synchronous Buck converter with integrated gate driver,” in *Proc. IEEE Energy Convers. Congr. Expo.*, 2014.
- [5] Y. Zhang, M. Rodriguez, D. Maksimovic, “Very high frequency PWM buck converters using monolithic GaN half-bridge power stages with integrated gate drivers,” *IEEE Trans. Power Electron.*, 2016.
- [6] A. Sepahvand, Y. Zhang, D. Maksimovic, “High Efficiency 20-400 MHz PWM Converters using Air-Core Inductors and Monolithic Power Stages in a Normally-Off GaN Process,” IEEE APEC 2016
- [7] Y. Zhang, J. Strydom\*, M. Rooij\*, D. Maksimovic, “Envelope Tracking GaN Power Supply for 4G Cell Phone Base Stations,” IEEE APEC 2016